

# Solving circuits with


12-Jan

## dependent current or voltage source

$R_{th}$   $V_{th}$


$R_N$   $I_N$

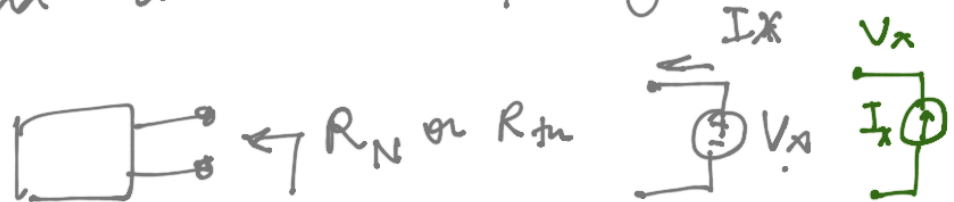- $R_{th}$ ,  $R_N$ . Apply test voltage  $V_x$  and find current  $I_x$  flowing through it.




$$R_N, R_{th} = \frac{V_x}{I_x} \leftarrow$$

- $V_{th}$ ,  $I_N$

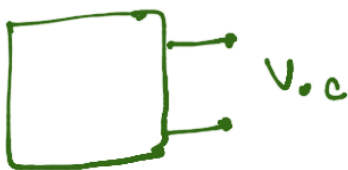

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

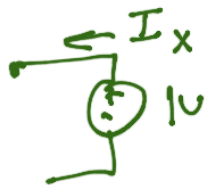

- ② Apply test voltage (1V) or current (1A) source.

$$R_{th} = \frac{1}{I_x} \left[ \text{when 1V test voltage applied} \right]$$

# RL & RC

Recap

$$\tau = \frac{L}{R}$$


R-L (no source)

$$I_L = I_0 e^{-\frac{R}{L}t}$$




R-L (Voltage Source)
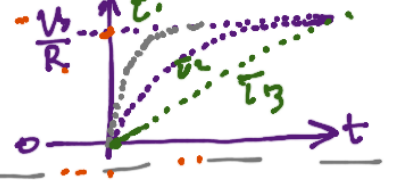
$$I_L = \frac{V_0}{R} (1 - e^{-\frac{R}{L}t})$$




R-C (no source)

$$V_C = V_{C0} e^{-\frac{t}{RC}}$$

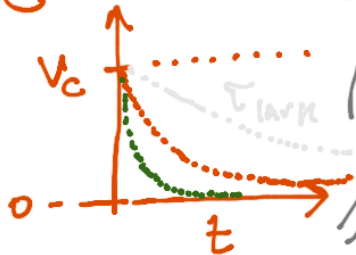

R-C (Voltage Source)

$$V_C = V_0 (1 - e^{-\frac{t}{RC}})$$

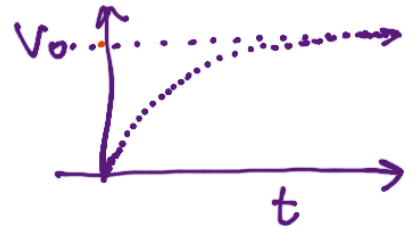

$\tau$  (time constant)

$$\tau = \frac{L}{R} \quad \text{'time' (R-L)}$$

fast decay. :  $\tau$  small  
slow response  $\tau$  large.

$$\tau = RC \quad \text{'time' (R-C)}$$

$\tau$  small  $\rightarrow$  fast  
 $\tau$  large  $\rightarrow$  slow

$$Fig. (\tau_1 < \tau_2 < \tau_3)$$

Characteristic equation :- Defines the circuit.

For any circuit let the following be its charc. equation

$$\frac{di}{dt} + Pi = Q \quad \left[ P, Q \rightarrow \text{constants} \right]$$

\* R-L or R-C type circuit will be 1<sup>st</sup> O.D.E

$$\frac{di + Pi dt = Q dt}{dt} : \text{--- (1)}$$

\*  $e^{-t/\tau}$

$e^{Pt} \rightarrow \text{integration}$

$$\textcircled{1} \Rightarrow \int e^{Pt} di + \int Pi e^{Pt} dt = \int Q e^{Pt} dt$$

$$\Rightarrow \int_0^t d(i e^{Pt}) = Q \int_0^t e^{Pt} dt$$

$$\Rightarrow i e^{Pt} = \int Q e^{Pt} dt + A$$

$$\Rightarrow i = \underbrace{e^{-Pt} \int Q e^{Pt} dt}_{\text{'i}_f \text{ Forced Response'}} + \underbrace{A e^{-Pt}}_{\text{'i}_n \text{ Natural / Transient'}}$$

↑ integration const

'Transient' = change with time

From prev. example:  $K_1 e^{-t/\tau}$  : Transient response  
(Even without  $V_s, I_s$ )

Natural Response of  
the circuit.

$$i_n = A e^{-pt}$$


Natural  $\uparrow$

- 'p' is 'ive R, L or C
- Natural response becomes '0' zero at  $t \rightarrow \infty$

Forced Response (F.R)

- Due to  $V_s$  or  $I_s$
- Final value after natural response die

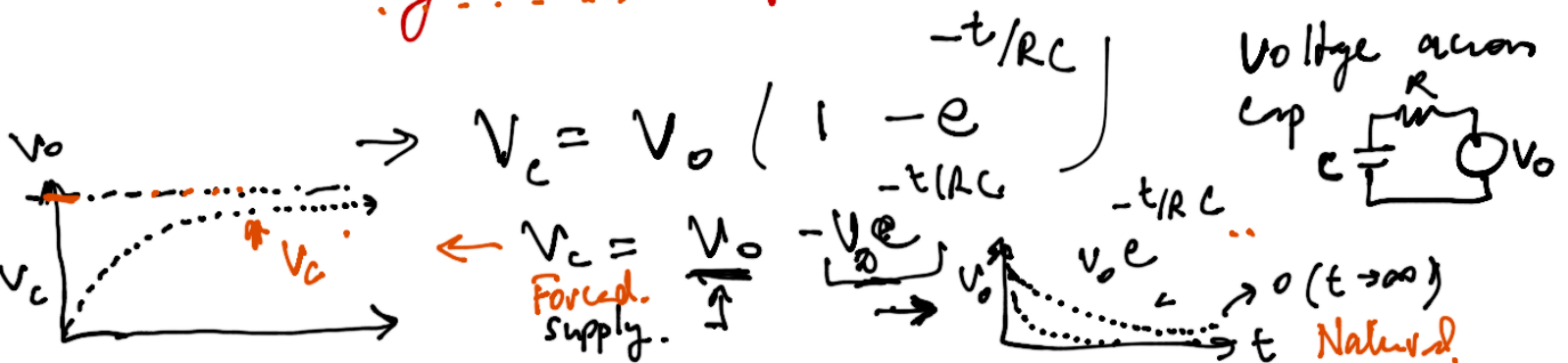F.R = Steady State Response. (s.s) (stays even  $t \rightarrow \infty$ )






# Response of a circuit





$$i = i_f + i_n$$
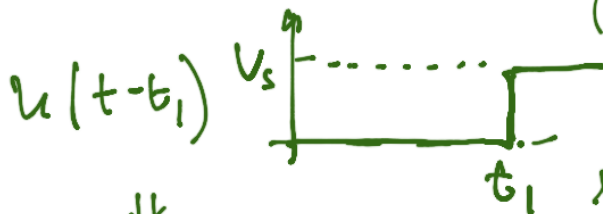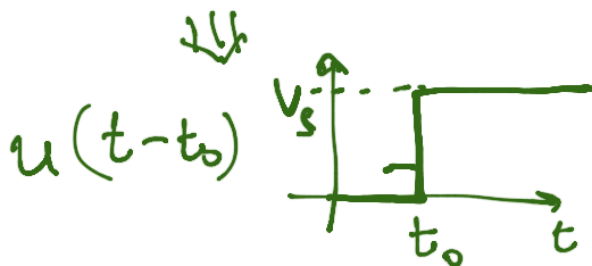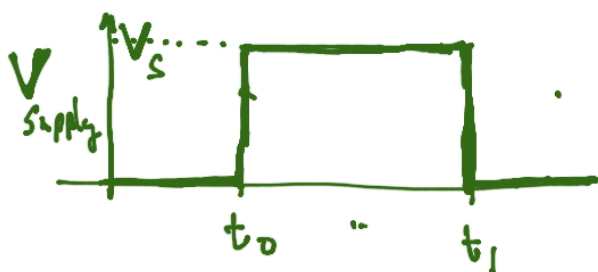
## Step Function



$$u(t) = \begin{cases} 0 & t < t_0 \\ V_s & t_0 < t < t_1 \\ 0 & t > t_1 \end{cases}$$




$$V_{supply} = u(t-t_0) - u(t-t_1)$$

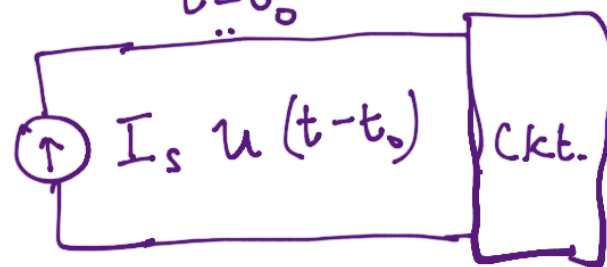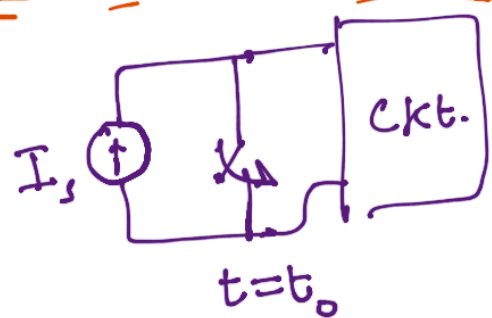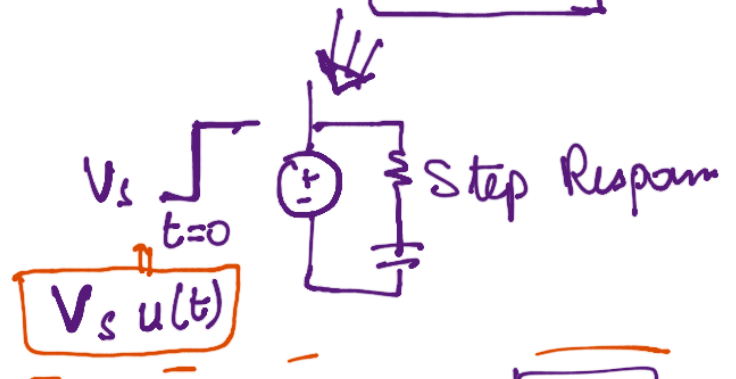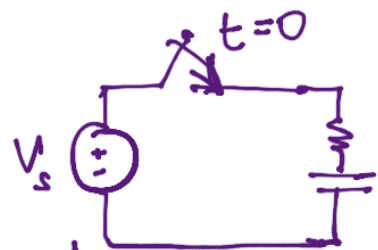


# Ex 8.2

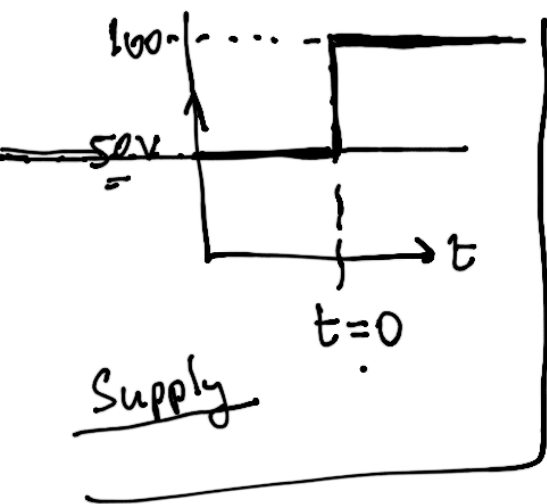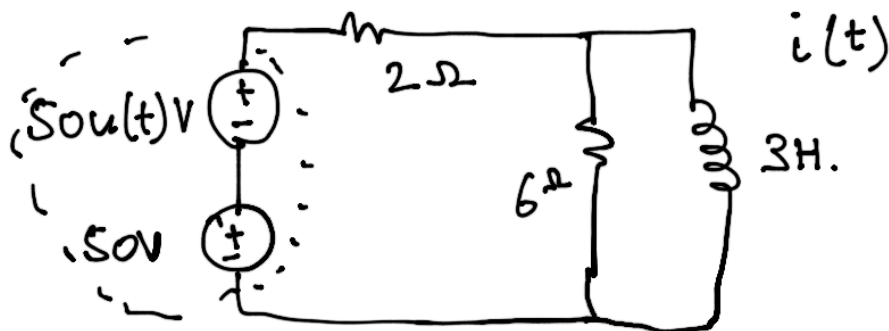

$t < 0$   
[for extremely long time]

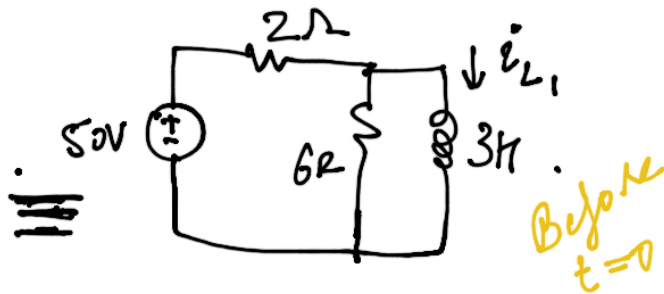


Inductor is like a S.C (short ckt)

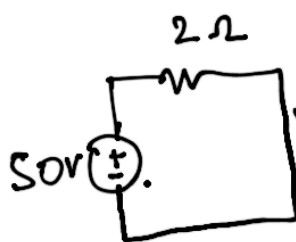


$$i_L = \frac{50}{2} = 25 \text{ A : initial condition}$$

After  $t > 0$

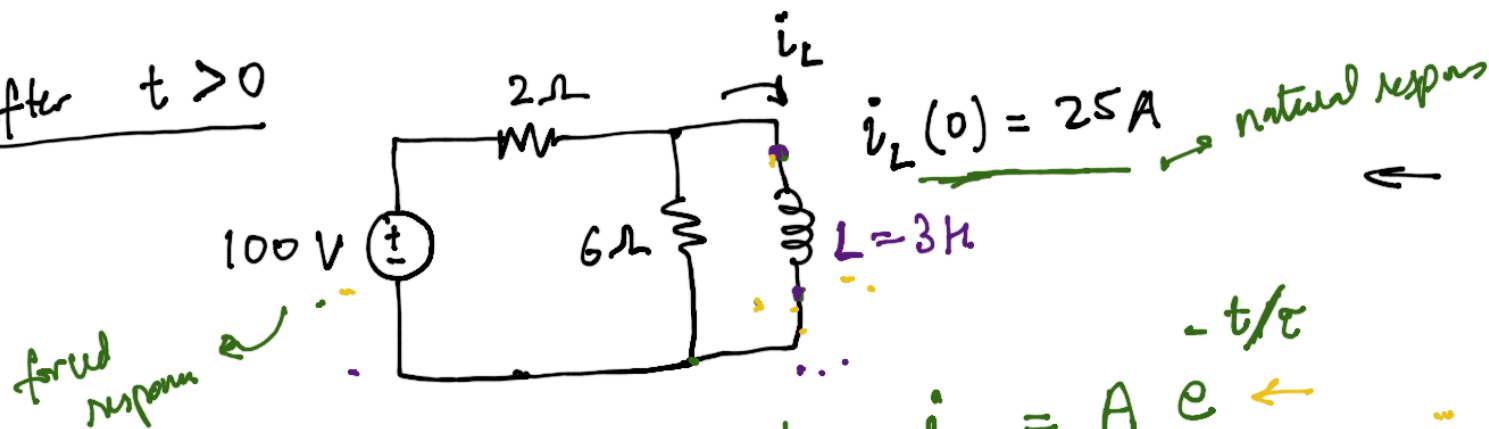

Let the Natural response be  $i_n = A e^{-t/\tau}$

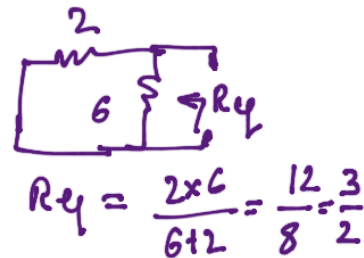
$$\tau : L = 3H, R_{eq} = \frac{3}{2}\Omega \Rightarrow \tau = \frac{L}{R} = \frac{3}{3/2} = 2 \text{ sec}$$



$$i_n = A e^{-t/2}$$

\$i\_f\$ : Natural part will die & constant or s.s current will remain.

the s.s.  
 $t \rightarrow \infty$

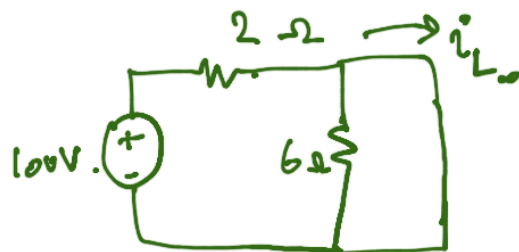

For forced response  
 $(t \rightarrow \infty) \quad L \rightarrow \text{s.c.}$

$$i_{L\infty} = \frac{100}{2} = 50 \text{ Amp.} \quad : \text{forced response}$$

$= i_f$  current in  $L$

General Total response

$$i_L = i_f + i_N \quad -t/2$$

$$i_L = 50 + A e^{-t/2} \quad \text{--- [A]}$$

$$t=0 \quad i_L(0) = 25 \text{ A}$$

$$i_L \Rightarrow 25 = 50 + A \Rightarrow A = -25$$

Finally putting 'A' back in [A]

$$i_L = 50 - 25 e^{-t/2}$$