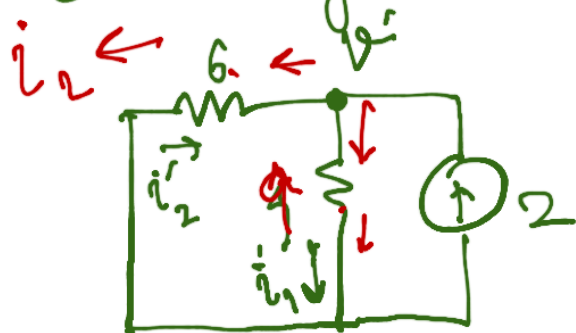


Sub 2

Keep  $i_{in}$  2A as it is

But voltage source  $V_{in}$  will be shorted




$$i_1' = \frac{6}{15} \times 2 = \frac{4}{5} A$$

$$i_2' = \frac{6}{5} A \checkmark$$

$$\frac{9}{6+9} \times 2$$

$$\frac{18}{15} = \frac{6}{5}$$

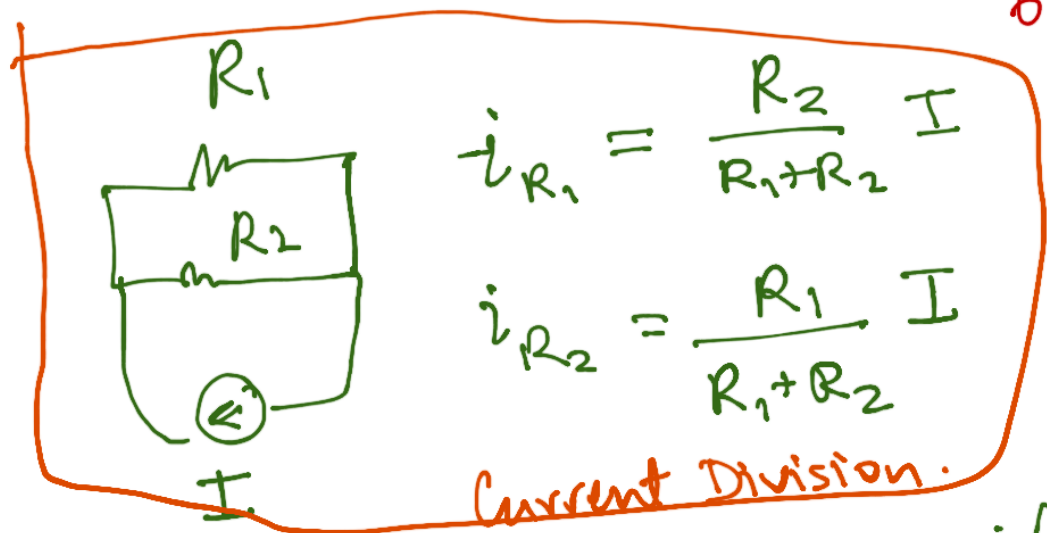

$$i_{R_1} = \frac{R_2}{R_1 + R_2} I$$

$$i_{R_2} = \frac{R_1}{R_1 + R_2} I$$

Current Division.

$$V' = i \times R = (\text{Branch 1 } 6\Omega) = 6\Omega \times i_2' = 6 \times \frac{6}{5} = \frac{36}{5}$$

$$= i_1' \times 9\Omega = \frac{4}{5} \times 9 = \frac{36}{5}$$

Net

	$V$	$i_1$	$i_2$
Sub 1	$\frac{9}{5}$	$\frac{1}{5}$	$\frac{1}{5}$
Sub 2	$\frac{36}{5}$	$\frac{4}{5}$	$\frac{6}{5}$
Total	$\frac{36+9}{5} = \frac{45}{5} = 9V$	$1A$ $(\frac{1}{5} + \frac{4}{5})$	$\frac{6+1}{5} = \frac{7}{5}$

(3V, 2A)

Ideal means = supplies  $i$  or  $V$  over time & for diff. load



$$i = \frac{5V}{50\Omega} = 0.1A$$

— ideal

$$i = 0.01A$$


$e^-$  lost energy = work done  
 $\Downarrow$   
 heat or light (W bulb)

$i$ ,  $V$ , energy.  
 $\downarrow$   $\downarrow$   
constant constant

$$E = \int i^2 R dt$$

Power will  $\downarrow$   $(0.1)^2 \times 50$   
 $(0.01)^2 \times 500$

# Source Resistance

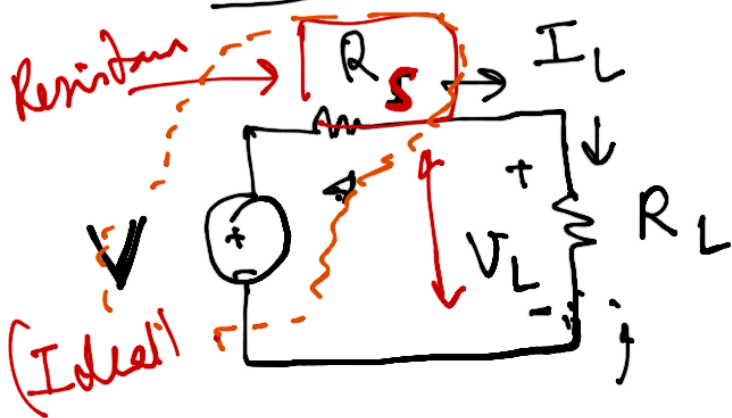

As we include wire resistance ( $R_s$ ) there is drop across it.

Suppose we increase  $I_L$ , drop across the  $R_s$  also increases.

	1 A	10 A	100 A
	$R_L$	$R_L$	$R_L$
Drop across $R_s$ only	$R_s$	$10 R_s$	$100 R_s$
What supply voltage across $R_L$ $V_L$	$V - 1 \cdot R_s$	$V - 10 R_s$	$V - 100 R_s$

Actual voltage seen by  $R_L$


$$V_L = V - I_L R_s$$

# Non ideal voltage source



- A real voltage is source whose (non ideal)

output / performance changes with load.

We non-ideal voltage source

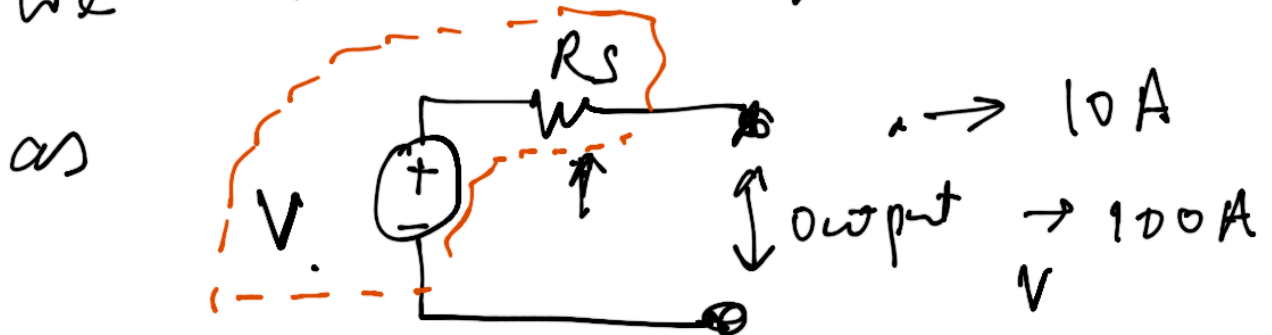

## Non ideal battery

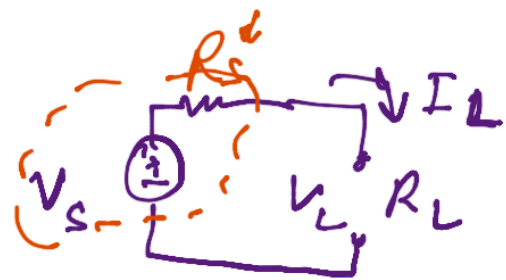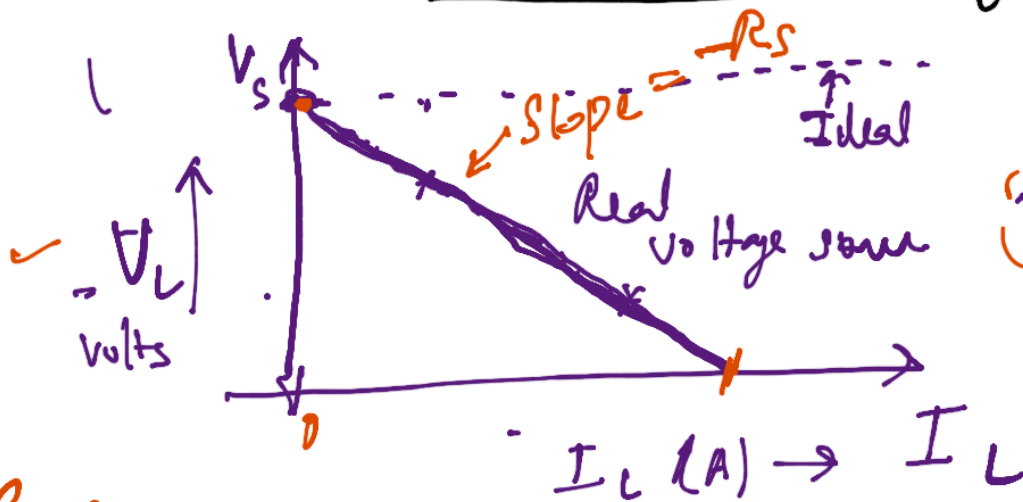


Voltage Source  
- Series

$R_s$  is source resistance


## Ideal current source

Supplies const. current for all loads

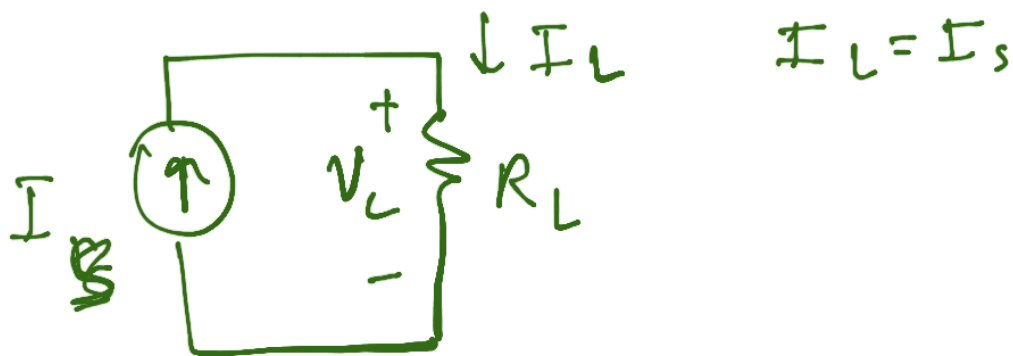

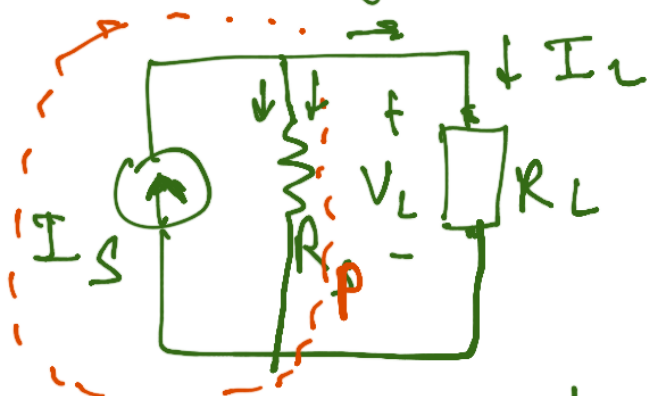
## Non ideal current source.




Supply current to load drops with increase in load.



$$I_L = I_s - \frac{V_L}{R_p}$$

Non ideal voltage source

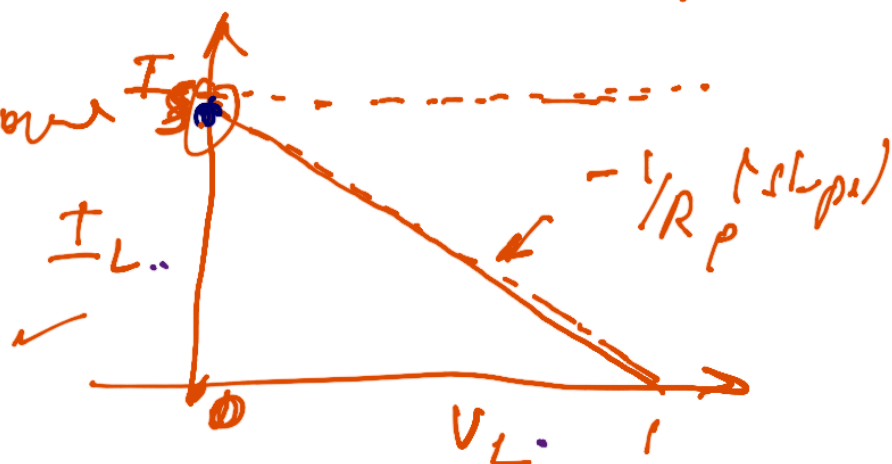


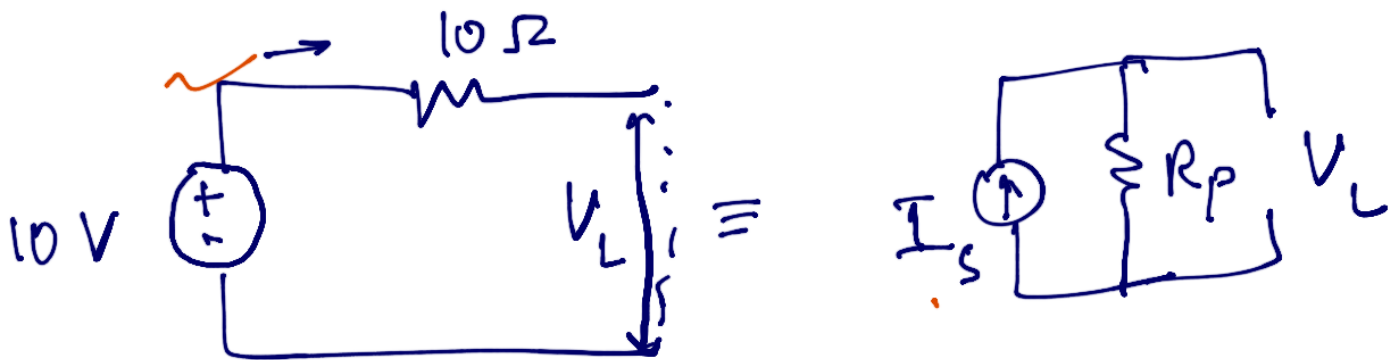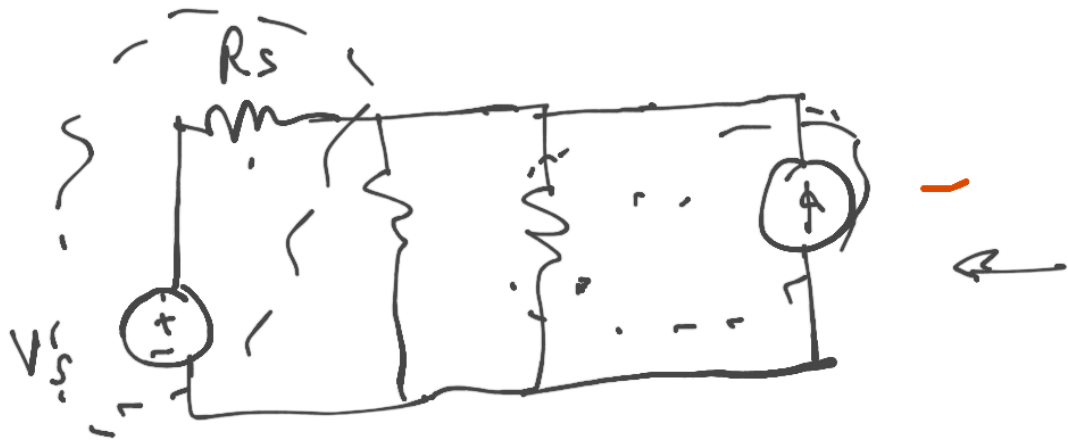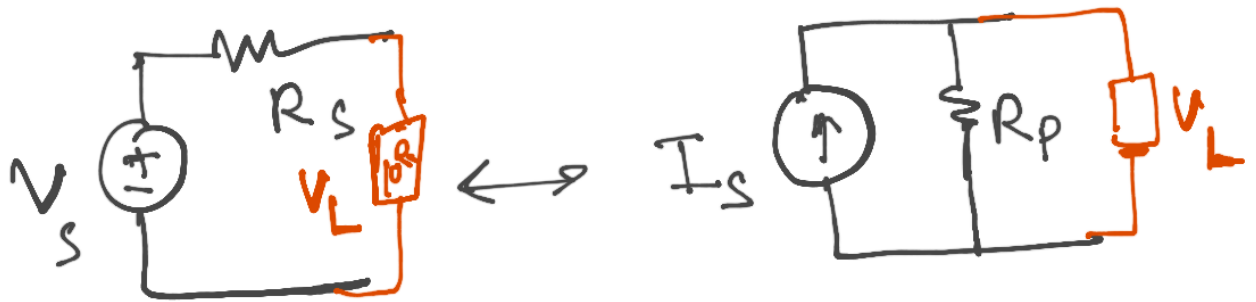

$$I_s = \frac{10V}{10\Omega} = 1A$$

[No load,  $V_L = 0$ ]

$$R_p = R_s$$

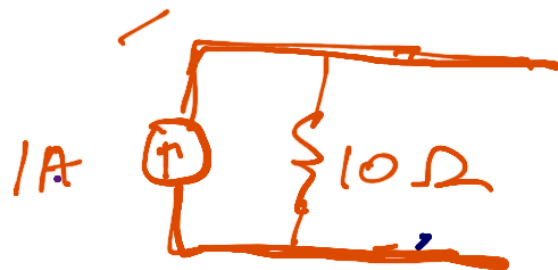

Current Source

$$\boxed{I_s, R_p} \Rightarrow \begin{cases} V_s = R_p I_s \\ R_s = R_p \end{cases}$$

Voltage Source

Voltage

$$\boxed{V_s, R_s} \Rightarrow \begin{cases} I_s = \frac{V_s}{R_s} \\ R_p = R_s \end{cases}$$

Current Source

Norton & Thvenin