

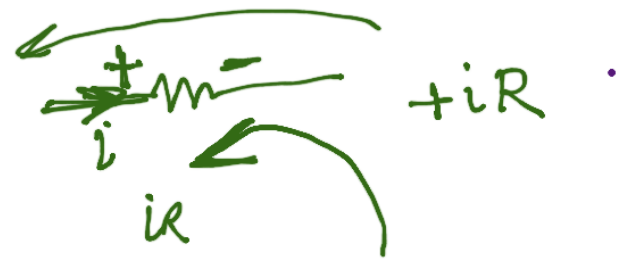



KVL

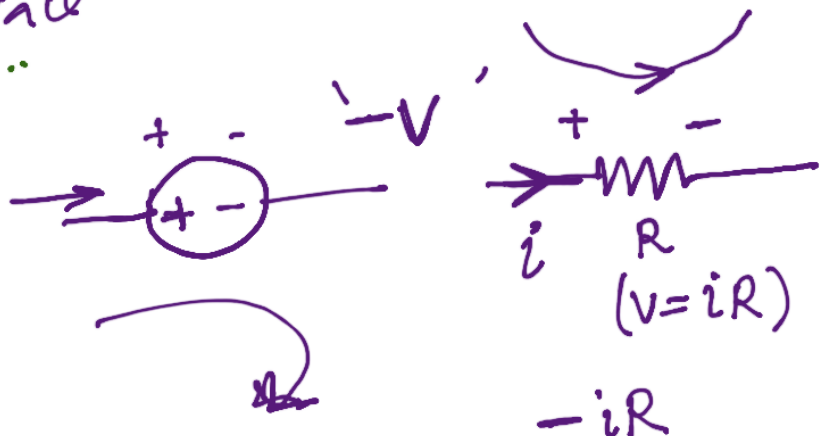1. Decide / select a loop .
2. Determine current direction.
3. Traverse loop & add (sub) voltages in the closed loop & equate it to zero.



Voltage : Add , subtract .
(KVL)

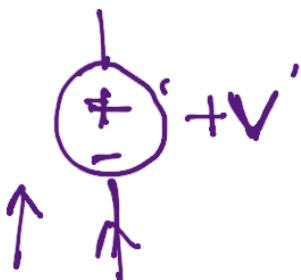


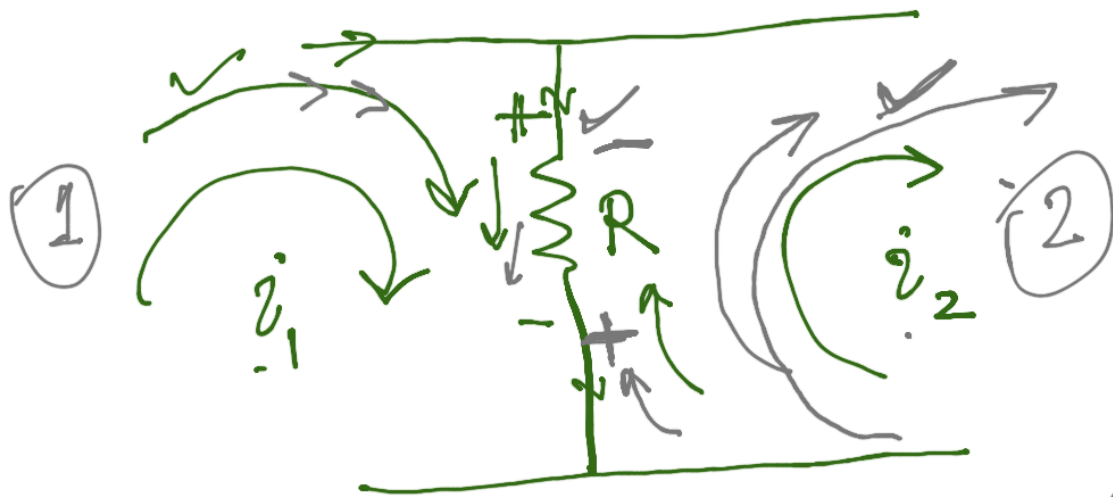

Drop : $-(i_1 - i_2)R$ (1) (Clockwise)

✓ $(i_2 - i_1)R$ ✓ $(i_1 - i_2)R$

$(i_2 - i_1)R$

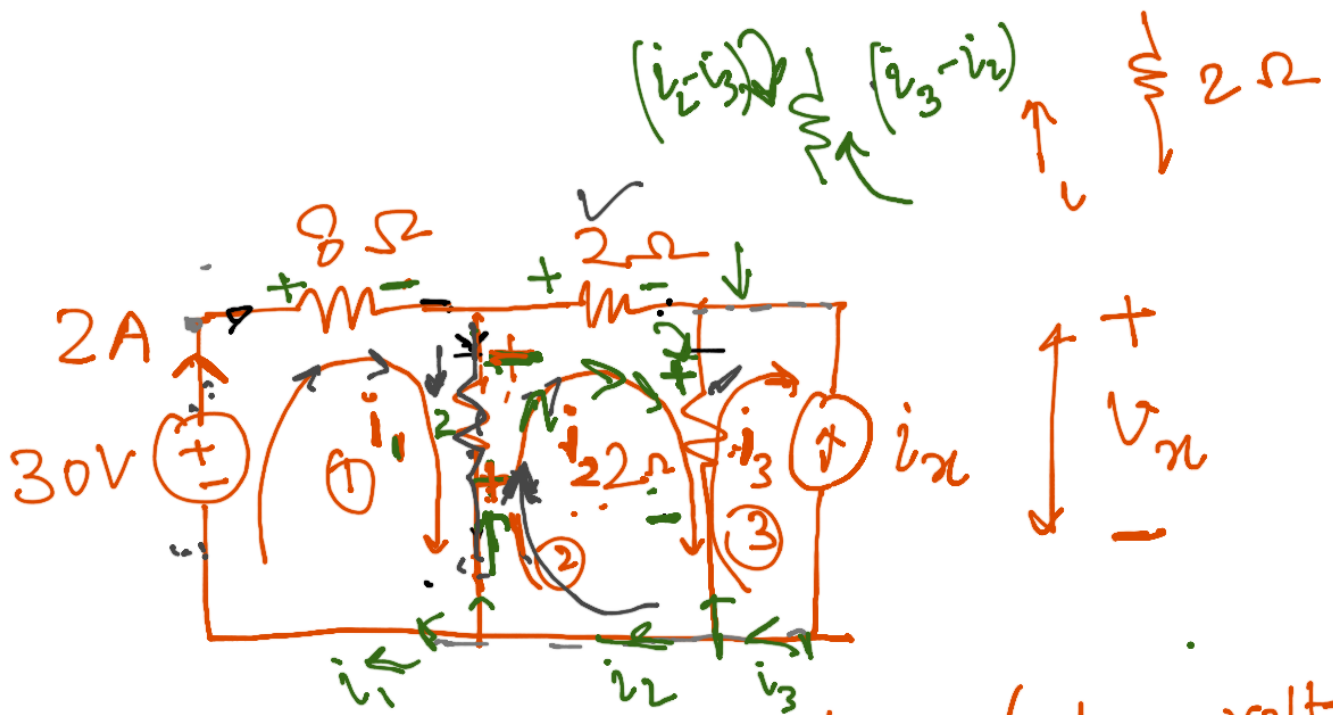

Step 1 Assume currents (drop-voltage!)
 3 loop currents. Direction of current flow: Clockwise. i_1, i_2, i_3

Determine voltage drop across 'R'.

Step 2 Traverse closed loop.


$\begin{matrix} - & + \\ \rightarrow & \end{matrix} \}$ Rise '+'
 $\begin{matrix} + & - \\ \rightarrow & \end{matrix} \}$ Drop '-'

$\rightarrow 2\Omega \text{ resistor: } (i_1 - i_2) R$
 $2\Omega \text{ " " : } (i_2 - i_3) R$

$\textcircled{L2} +30 - 8 \times i_1 - 2(i_1 - i_2) = 0$
 $\textcircled{L2} +2(i_1 - i_2) - 2i_2 - 2(i_2 - i_3) = 0$
 $\textcircled{L2} -2(i_2 - i_1) - 2i_2 - 2(i_2 - i_3) = 0$
 $\textcircled{L3} -2(i_3 - i_2) - V_x = 0 \Rightarrow +2(i_2 - i_3) - V_x = 0$


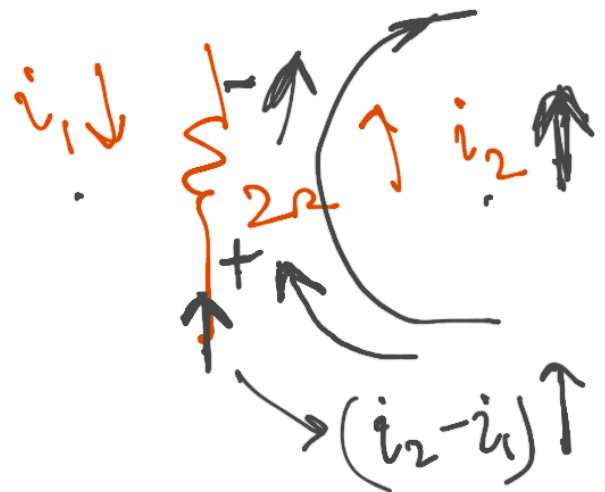
$$V_R = \frac{2(i_1 - i_2)}{\text{Net current} \downarrow}$$




$$V_R = 2(i_2 - i_1)$$

What is the direction of $i_{\text{net current loop}}$
 in the component during traversal.

Steps: KCL

KCL

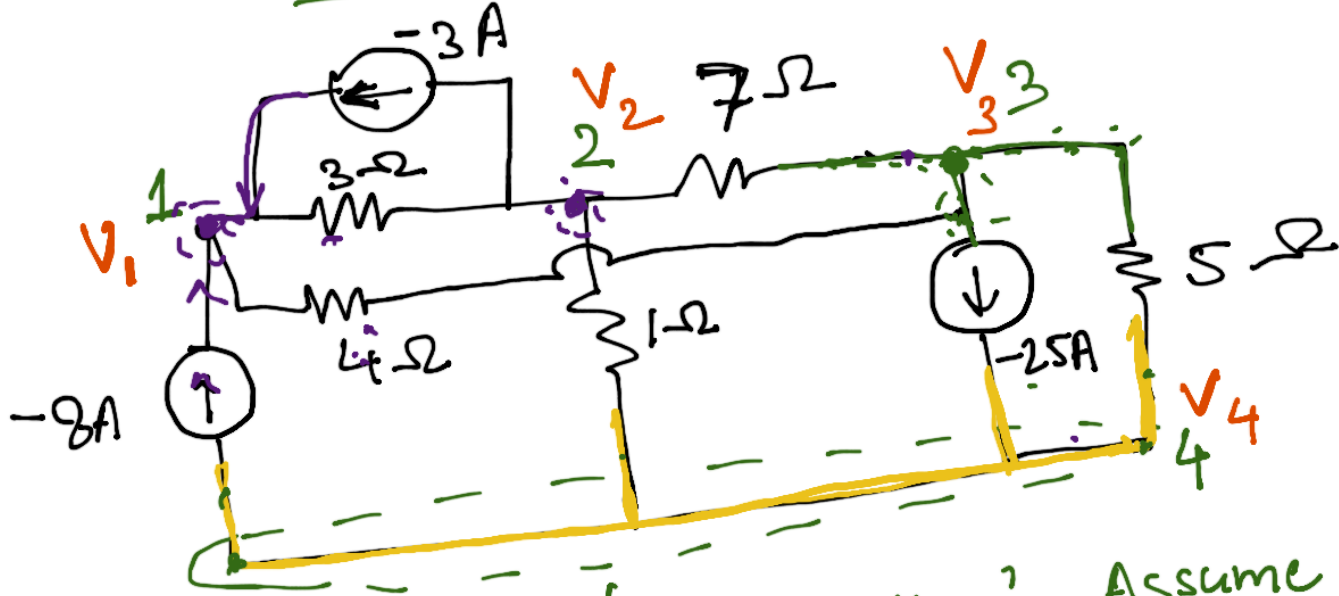

1. Identify Nodes. 'Node voltage'. Assume Node voltage.

2. Determine current flow

3. Write equation at node $\sum i = 0$

(N1) KCL $-8A - 3A + \frac{V_2 - V_1}{3} + \frac{V_3 - V_1}{4} = 0$ ①

$-8A - 3 = \frac{V_1 - V_2}{3} - \frac{V_1 - V_3}{4} = 0$

N2, N3, N4

$V_1 \quad V_2 \quad V_3 \quad V_4$