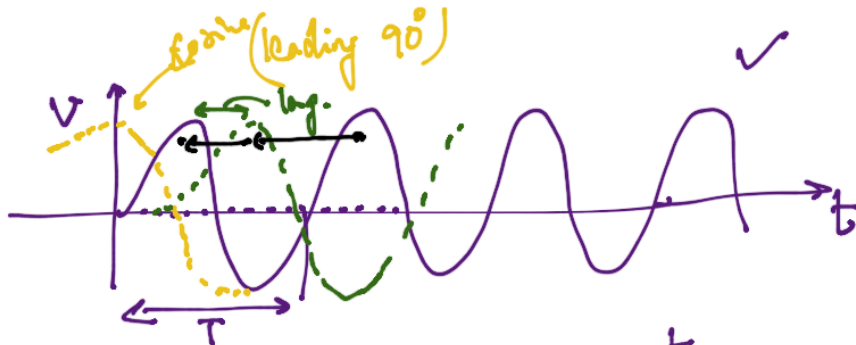


25 Jan

V source $\left\{ \begin{array}{l} V \text{ constant } \checkmark \text{ Battery, } \checkmark \\ V(t) = V e^{-kt} \rightarrow \text{Input.} \leftarrow \text{first principle.} \end{array} \right.$



$$V = V_m \sin \omega t$$

$$f = \frac{1}{T}$$

$$\omega = 2\pi f = \frac{2\pi}{T}$$

$\omega \rightarrow 2\pi f$
 $f \rightarrow 50 \text{ Hz (India)}$
 $f = 60 \text{ Hz (U.S.)}$



$$V_1 = V_{m1} \cos(\omega t + 10^\circ)$$

$$= V_{m1} \sin(\omega t + 90^\circ + 10^\circ)$$


$$V_2 = V_{m2} \sin(\omega t - 30^\circ)$$

V_1 is leading V_2 by $(90 + 10 + 30) = 130^\circ$

$$360^\circ - 180^\circ = 180^\circ$$

$\rightarrow V_1$ is lagging V_2 by $180^\circ - 130^\circ = 50^\circ$

rad.
or
degree

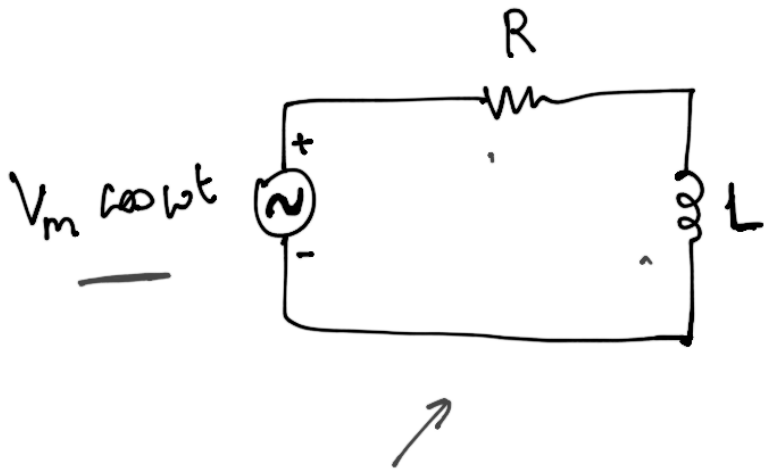

$$V_R + V_L = V_s$$

$$iR + L \frac{di}{dt} = V_m \cos \omega t \quad \text{--- [1]}$$

↓
solution

$$i = I_1 \cos \omega t + I_2 \sin \omega t \quad \text{--- [2]}$$

Substitute [2] in [1]

$$(I_1 \cos \omega t + I_2 \sin \omega t) R + L \frac{d}{dt} (I_1 \cos \omega t + I_2 \sin \omega t) = V_m \cos \omega t$$

$$\Rightarrow \cos \omega t [I_1 R + \omega L I_2 - V_m] + [I_2 R - I_1 L \omega] \sin \omega t = 0$$

Coeff. of sine & cosine have to $= 0$

$$\left. \begin{aligned} I_1 R + \omega L I_2 - V_m &= 0 \quad \text{--- [3]} \\ I_2 R - I_1 L \omega &= 0 \quad \text{--- [4]} \end{aligned} \right\} I_1 \text{ & } I_2 \rightarrow \text{unknown}$$

Solve [3] & [4] simultaneously $I_1 = \frac{R V_m}{R^2 + \omega^2 L^2}$

$$I_2 = \frac{\omega L V_m}{R^2 + \omega^2 L^2}$$

$$i = \frac{R V_m}{R^2 + \omega^2 L^2} \cos \omega t + \frac{\omega L V_m}{R^2 + \omega^2 L^2} \sin \omega t \quad \text{--- [5]} = A \cos(\omega t + \theta)$$

Further converting [5] into 'cos'

$$[6] \quad \underline{A \cos(\omega t + \theta)} = \underbrace{A \cos \omega t \cos \theta} - \underbrace{A \sin \omega t \sin \theta}$$

From [5] $\cos \theta$ & $\sin \theta$

$$\Rightarrow \tan \theta = \frac{\omega L}{R}$$

$$\Rightarrow \theta = \tan^{-1} \frac{\omega L}{R}$$

Comparing [5]
with [6]

Using $(A \cos \theta)^2 + (A \sin \theta)^2 = A^2 \Rightarrow [6]$


$$= \left[\frac{(R V_m)^2 + (\omega L V_m)^2}{(R^2 + \omega^2 L^2)^2} \right] = \text{Using [5]}$$

$$= \frac{V_m^2 \cdot 1}{R^2 + \omega^2 L^2} = A^2 \Rightarrow A = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\Rightarrow i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \theta)$$

$\theta = \tan^{-1} \frac{\omega L}{R}$

27 Jan

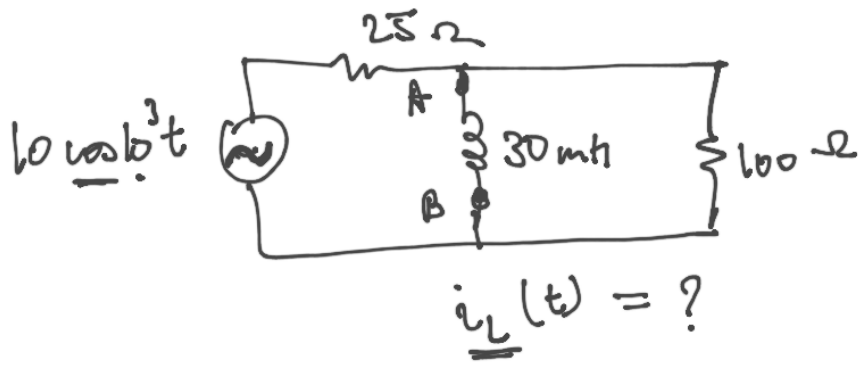

Method 1 $I_s \rightarrow V_L, V_R$

$V_s \rightarrow I_s$

- AC
- Phasor



AC power.

[2 port
Op-amp
Dual limit]

Method 2 Find Thevenin voltage and resistance

across \downarrow

(30 mH $\rightarrow Z_{L \text{ load}}$)

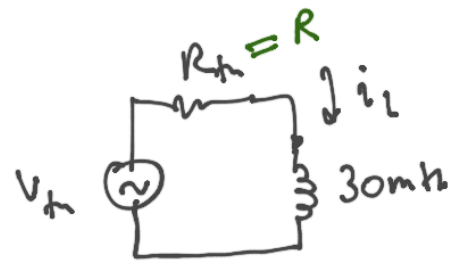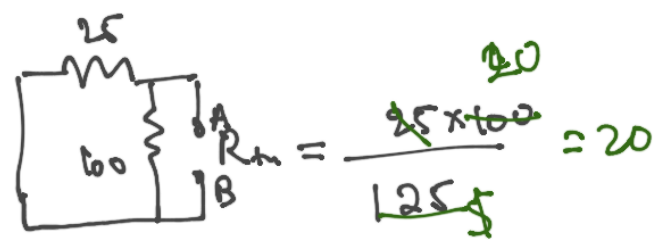

$$i_L(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi)$$

$$\phi = \tan^{-1} \frac{\omega L}{R}$$

$$i_L(t) = \frac{\frac{100}{125} \times 10}{\sqrt{20^2 + (10^3)^2 (30 \times 10^{-3})^2}} \cos(10^3 t + \tan^{-1} \frac{2}{3})$$

$$\cos\left(10^3 t + \tan^{-1} \frac{2}{3}\right)$$

Complex forcing function

$$\underline{V_m \cos(\omega t + 0^\circ)} = \underline{V_m \angle 0^\circ}$$

sinusoidal function ' ωt '

$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$

$\left[\theta \rightarrow \text{any phase} \right]$

$$\underline{V_m \cos(\omega t + \theta)} = \text{Re} \left[\underline{V_m e^{j\omega t + \theta}} \right]$$
$$= \text{Re} \left[V_m \angle \theta \right]$$

→ 2 part stimulus: Re , Im .

\downarrow \downarrow

$\cos \omega t$ $j \sin \omega t$

By principle of superposition $[L, R, C, V_s, I_s \rightarrow \text{linear}]$

The output will also be a sum of Re & Im

Input $\rightarrow V_m (\cos \omega t + j \sin \omega t) \xrightarrow{\quad} e^{j\omega t}$

Output $\rightarrow I_m (\cos(\omega t + \phi) + j \sin(\omega t + \phi)) \leftarrow$

$\left[\begin{array}{l} \text{Imaginary sources cause Im response} \\ \text{Real sources cause Re response} \end{array} \right]$


$$V_m \cos(\omega t + \theta)$$

Step 1 $V_m e^{j(\omega t + \theta)}$

Step 2 $\frac{I_m e^{j(\omega t + \phi)}}{\quad}$


$V_o e^{j(\omega t + \phi')}$
 $I_m \rightarrow \text{Amplitude}$

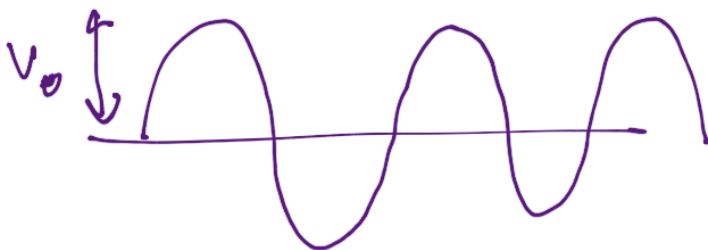final output: $\text{Re} [I_m e^{j(\omega t + \phi)}]$



$$V_o \sin \omega t$$

Ex 10.2

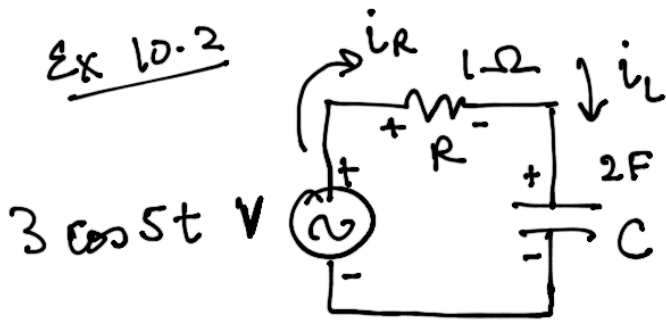

Solve 'steady-state' cap volt.
 V_C

$$\rightarrow 3 \cos 5t \Rightarrow \text{Re}[3 e^{j5t}]$$

↓
forcing function.

KVL $V = V_R + V_C$

$$3 e^{j5t} = i_R R + V_C$$

$$i_C = C \frac{dV_C}{dt} = i_R$$

$$3 e^{j5t} = RC \frac{dV_C}{dt} + V_C \quad \text{--- [A]}$$

$j(5t + \phi)$

Solution V_C will be of the form $V_C = \underline{V_m e^{j(5t + \phi)}}$

[A] \Rightarrow $3 e^{j5t} = RC V_m (j5) e^{j(5t + \phi)} + V_m e^{j(5t + \phi)}$

$$3 = RC V_m (j5) e^{j\phi} + V_m e^{j\phi}$$

$$3 = (jRC V_m 5 + V_m) e^{j\phi}$$

$$V_m = \left(\frac{3}{1 + j5RC} \right) e^{-j\phi} = \left(\frac{3(1 - j5RC)}{1 + (5RC)^2} \right) e^{-j\phi}$$

$$V_m = \frac{3(1 - j5RC)}{1 + (5RC)^2} e^{-j\phi}$$

$$\text{phase} = \tan^{-1}\left(\frac{-5RC}{1}\right) = \tan^{-1}(-10) = -84^\circ$$

$\nwarrow \omega RC$
 $\nwarrow (\text{check!})$

$$\text{Amplitude} = \frac{3}{\sqrt{1 + 10^2}} = 0.3 \text{ (approx)}$$

Solution \rightarrow

$$V_c = 0.3 \tan^{-1}(-10) = 0.3 \text{ phase } (-84^\circ)$$

$$V_c = 0.3 \underbrace{e^{j5t}}_{\downarrow} e^{-j84^\circ}$$


coming from forcing function

$$\text{Voltage across the capacitor is } \text{Re}\left[0.3 e^{j(5t - 84^\circ)}\right]$$

* No differential equation in time was solved.

* Solution was done in freq. domain 'wt'.

In General form

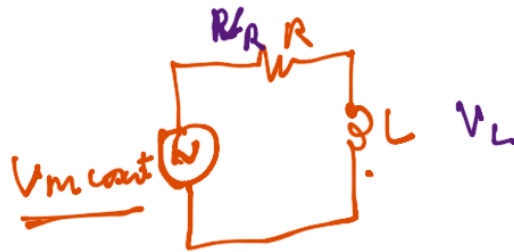

$$V_{\text{source}} = Ri + L \frac{di}{dt}$$

Step 1 Complex exp. source $V_m e^{j\omega t} = V_m \angle 0^\circ (\omega)$

Step 2 Response will be $i = I_m e^{j(\omega t + \phi)}$

Step 3 Write KVL (or KCL) \Rightarrow differential equation
'C' or 'L'

Step 4 Substitute solution $i(t) = I_m e^{j(\omega t + \phi)}$

Step 5 Solve the Diff. eqⁿ with $I_m e^{j(\omega t + \phi)}$

$$Ri + L \frac{di}{dt} = V_m e^{j\omega t}$$

$$\text{LHS} = R I_m e^{j(\omega t + \phi)} + L(j\omega) I_m e^{j(\omega t + \phi)}$$

$$V_m = R I_m e^{j\phi} + j\omega L I_m e^{j\phi}$$

$$= (R + j\omega L) \underline{I_m} e^{j\phi}$$

$$I_m e^{j\phi} = \frac{V_m}{R + j\omega L} \rightarrow \text{Mag \& phase}$$


$$I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \quad \tan^{-1} \frac{\omega L}{R}$$

Step 6 Express $I_m e^{j\phi}$ in terms of V_m, R, ω, L

Solution: $I_m e^{j\phi} = I_m e^{j(\omega t + \phi)} \Rightarrow I_m \angle \phi (\omega) \Rightarrow \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle \tan^{-1} \omega L / R$

$$I_m \angle \phi : \underline{\text{Phasor representation.}}$$

Phase
↓
phasov

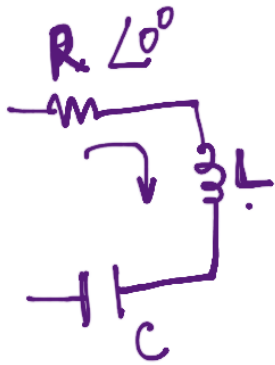

$$RGL: \phi = \tan^{-1} \left(-\frac{\omega L}{R} \right) \leftarrow$$

R & C: $\phi = \tan^{-1}(\omega RC)$ ←

Inductor

$$V_L = L \frac{di}{dt}$$

$$\text{let } \underline{i} = I_m e^{j(\omega t + \phi)}$$

$$V_L = I_m(j\omega)L e^{j(\omega t + \phi)}$$


$$V_L = V_m e^{j(\omega t + \theta)} = j\omega L I_m e^{j(\omega t + \phi)}$$

$$\Rightarrow \underline{V} (V_m e^{j\theta}) = j\omega L (\underline{I} (I_m e^{j\phi}))$$

Amp of voltage across Ind = $j\omega L$
for a current $I_m e^{j\phi}$

$$V = j\omega L I$$
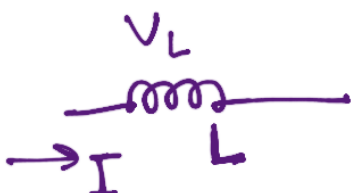
$$\underline{V} = j\omega L = \text{Impedance}$$



Capacitor

$$i_c = C \frac{dv_c}{dt}$$

$$v_c = V_m e^{j(\omega t + \phi)}$$


$$i_c = C V_m j \omega e^{j(\omega t + \phi)}$$

$$I_m e^{j(\omega t + \theta)} = j \omega C V_m e^{j \omega t + \phi}$$

$$\frac{I_m e^{j\theta}}{I} = j \omega C \frac{V_m e^{j\phi}}{V}$$

$$I = j \omega C V$$

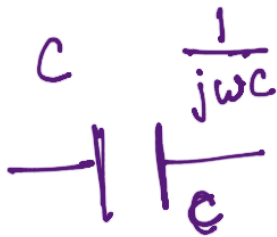
$$\Rightarrow \frac{V}{I} = \text{Impedance of Capacitor} = \frac{1}{j \omega C}$$



Resistor no V_R & $I_R \rightarrow$ no lag \therefore 'R'


Time Domain

Frequency Domain

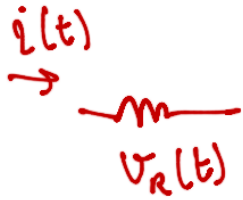



$$v_R(t) = R i(t)$$

$$V = RI$$

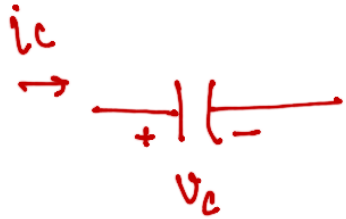

$$v_C = \frac{1}{C} \int i_C dt$$

$$V = \frac{I}{j\omega C}$$

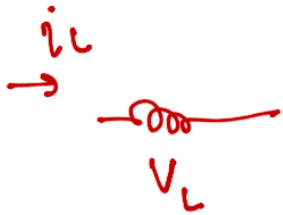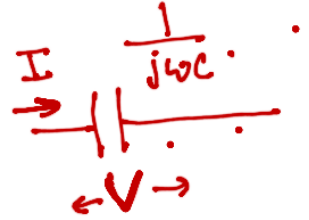


$$v_L = L \frac{di_L}{dt}$$

$$V = j\omega L I$$




Ex 10.5

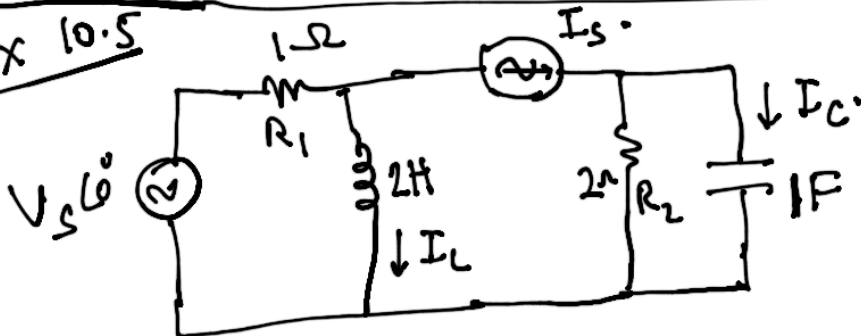

Q: I_S & $i_C(t) = ?$

$$\omega = 2 \text{ rad/s}$$

$$I_C = 2 \angle 28^\circ \text{ A}$$

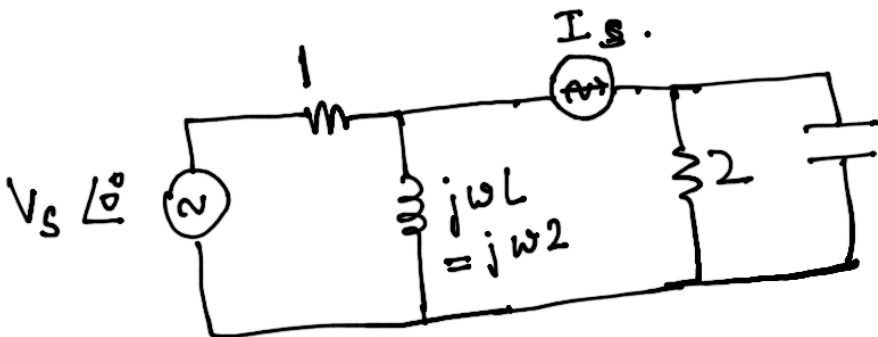


$$\frac{1}{j\omega C} = \frac{1}{j\omega 1}$$

Apply:

Z is series $Z_1 + Z_2$

Z in || $\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$

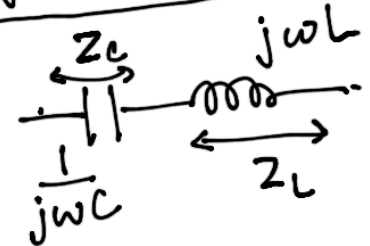

$$\begin{aligned} Z &= Z_C + Z_L \\ &= \frac{1}{j\omega C} + j\omega L = \frac{-j}{\omega C} + j\omega L \\ &= j \left(\omega L - \frac{1}{\omega C} \right) \end{aligned}$$