

# RLC Circuits

22 Jan

(From char eq<sup>n</sup>)

$$s = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\alpha = \text{Damping coefficient} = \frac{1}{2RC}$$

$$\omega_0^2 = \frac{1}{LC} = \text{Resonant frequency}$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

	$\alpha^2 - \omega_0^2$	$s_1$	$s_2$	Name
$\alpha > \omega_0$	+	-	-	Over damped
$\alpha = \omega_0$	0	$-\alpha$	$-\alpha$	Critical Damping
$\alpha < \omega_0$	-	$-\alpha + j\omega_d$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$	$-\alpha - j\omega_d$	Under damped

Overdamping

$$\alpha^2 > \omega_0^2$$

$$\Rightarrow \frac{1}{(2RC)^2} > \frac{1}{LC}$$

$$\Rightarrow \frac{1}{4R^2C^2} > \frac{1}{LC}$$

$$\Rightarrow L > 4R^2C$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

Real

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Real

$$v = A e^{s_1 t} = A e^{s_1 t} + B e^{s_2 t} \quad \text{[Natural Response]}$$

$$v_n = A e^{-t/\tau_1} + B e^{-t/\tau_2}$$

Time constants

$$\tau_1 = \frac{1}{s_1}$$


$$\tau_2 = \frac{1}{s_2}$$

$$|s_1| < |s_2|$$

$$\Rightarrow \tau_2 < \tau_1$$

$$V = V_f + V_n$$

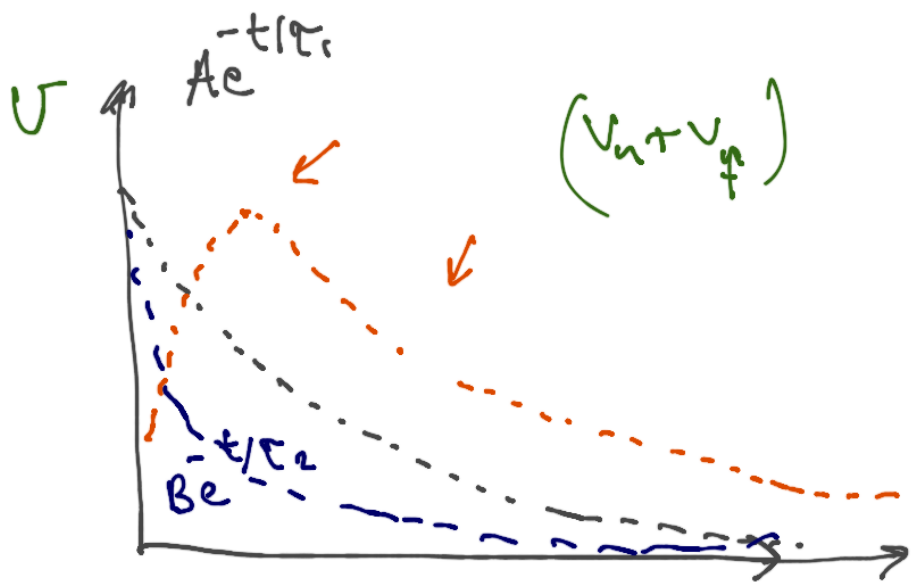↓                      ↓  
at  $t \rightarrow \infty$



Critical Damping.

$$\alpha^2 = \omega_0^2$$


$$\left(\frac{1}{2RC}\right)^2 = \frac{1}{LC}$$

$$\boxed{L = 4R^2C} \quad \text{Critical Damp.}$$

Solution  $s_1, s_2 = -\alpha$   $\rightarrow V_n = C e^{-\alpha t} + D t e^{-\alpha t}$

$\rightarrow V_n = (C + Dt) e^{-\alpha t}$

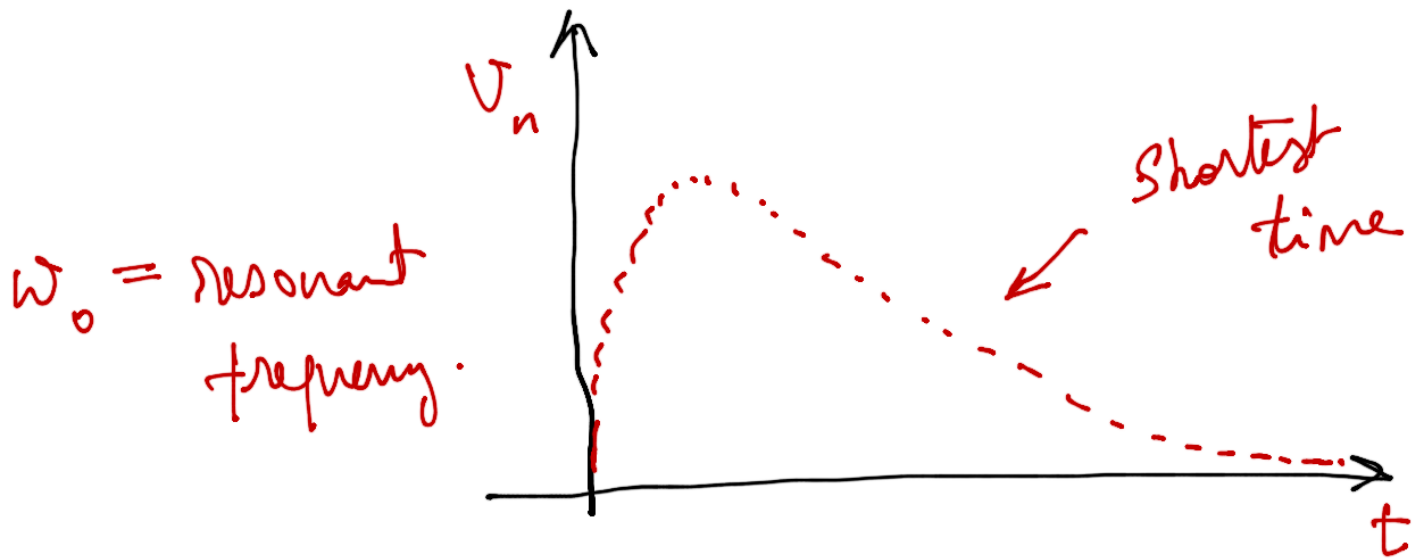↑ [Math. sol  
2nd ODE  
with same  
roots]



$$V = V_f + V_n$$

Under damping.

$$\alpha < \omega_0 \Rightarrow \left(\frac{1}{2RC}\right)^2 < \frac{1}{LC}$$

$$\Rightarrow \boxed{L < 4R^2C}$$

$$S_1 = -\alpha + j\omega_d$$

$$S_2 = -\alpha - j\omega_d$$

$$\omega_d^2 = \omega_0^2 - \alpha^2$$

$S_1, S_2 \rightarrow$  Complex numbers

$j \rightarrow$  Imaginary  $\sqrt{-1}$

$$V_n = A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$


Natural Complete Solution

$$\left( \cos \omega_d t + j \sin \omega_d t \right) \quad \left( \cos \omega_d t - j \sin \omega_d t \right)$$


$$V_n = e^{-\alpha t} \left( B_1 \cos \omega_d t + B_2 \sin \omega_d t \right)$$

$B_1, B_2 \rightarrow$  constant. [initially condition]

Under Damping.

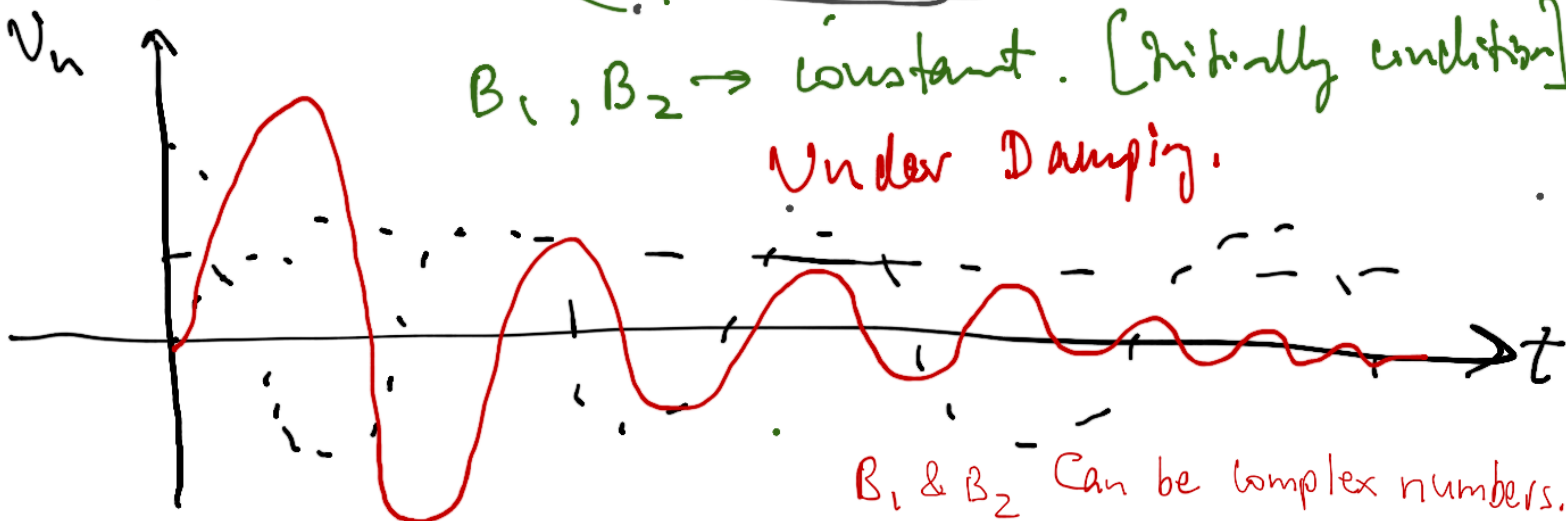

$B_1$  &  $B_2$  Can be complex numbers.

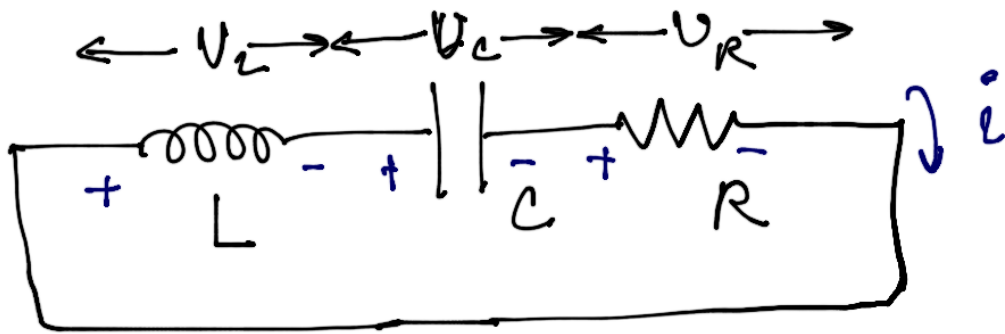

Natural response of SERIES R-L-C

KVL  $V_L + V_C + V_R = 0$

$$L \frac{di}{dt} + \frac{1}{C} \int i dt + iR = 0$$

$$\underbrace{V_L = L \frac{di}{dt}} \quad \underbrace{i_C = C \frac{dV_C}{dt}}$$

Taking derivative wrt 't'

$$\Rightarrow L \frac{d^2 i}{dt^2} + \frac{1}{C} i + R \frac{di}{dt} = 0$$

2<sup>nd</sup> ODE in 'i'

Characteristic  
Eq<sup>n</sup>

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} = 0$$

As we know sol<sup>n</sup>  $i = A e^{st}$

Substitute back in charac. eq<sup>n</sup>.

$$\underbrace{\left( s^2 + \frac{R}{L}s + \frac{1}{LC} \right)}_{\text{quad eq}^n} A e^{st} = 0$$

$$\underline{\text{Sol:}} \quad s = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

$$\alpha = \text{Damping coefficient} = \frac{R}{2L}$$

$$\omega_0 = \text{Charac. frequency} = \frac{1}{\sqrt{LC}}$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


3 solution

	$\alpha^2 - \omega_0^2$	$s_1$	$s_2$	
$\alpha > \omega_0$	+	Real	Real	Overdamped
$\alpha = \omega_0$	0	$-\alpha$	$-\alpha$	Critically damped.
$\alpha < \omega_0$	Imaginary	$-\alpha \pm j\omega_d$	$-\alpha \pm j\omega_d$	Under damped.
		$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$		

Overdamped case

Solution:

$$i_n = A_1 e^{s_1 t} + B e^{s_2 t}$$

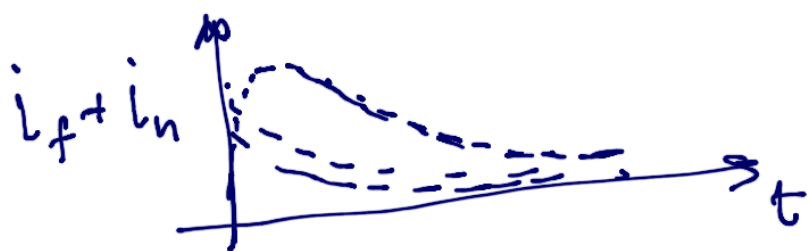


$$\alpha^2 > \omega_0^2$$

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

$$2 < \frac{R^2 C}{L}$$

Critically case


$$i_n = (A + Bt) e^{-\alpha t}$$

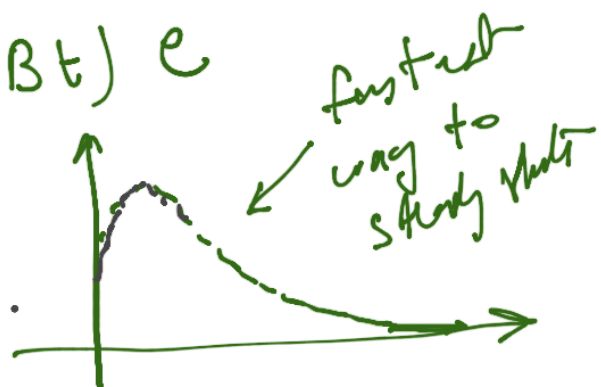



Under damped  
 $\alpha < \omega_0$

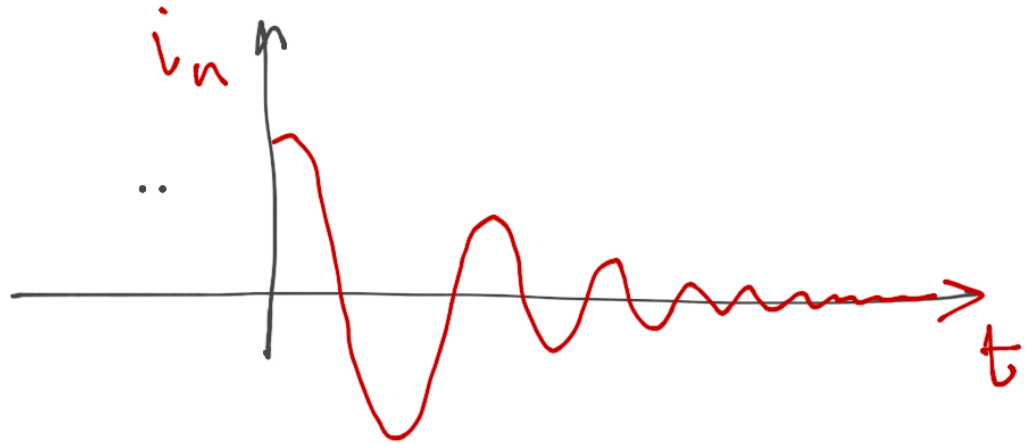
$$i_n = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$



# Ex 9.6


$$\begin{matrix} 3A & t < 0 \\ 0 & t > 0 \end{matrix}$$

$$3u(-t)A$$

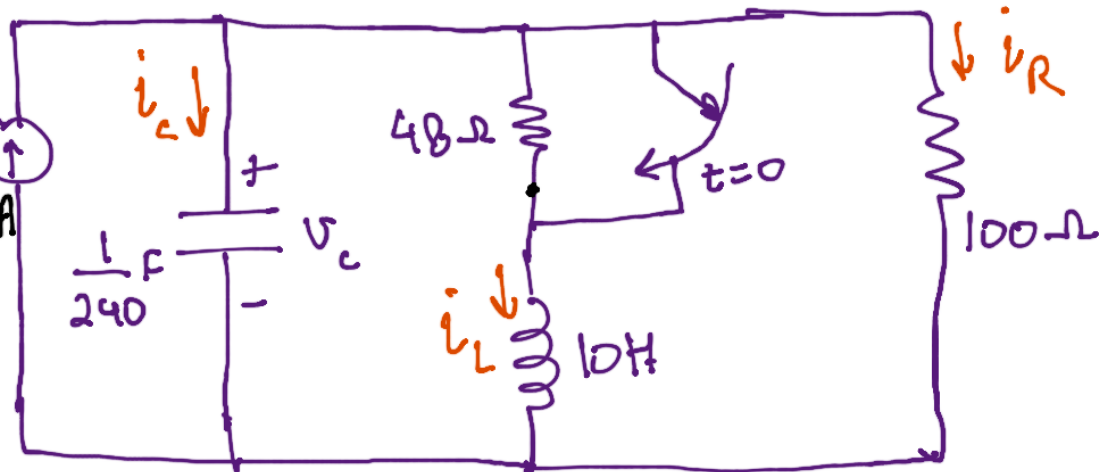

$$i_L(t) = ?$$

$t > 0$

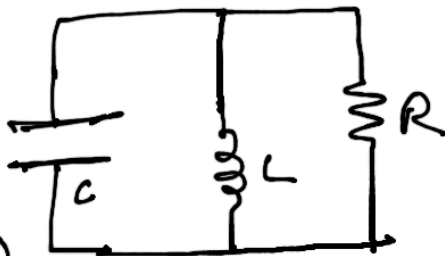

CKT A

$$C = \frac{1}{240} \quad R = 100 \quad L = \frac{1}{10}$$

$$\checkmark \alpha = \frac{1}{2RC} = 1.2$$

$$\checkmark \omega_0 = \frac{1}{\sqrt{LC}} = 5$$

$$\alpha < \omega_0$$

Under damped.

$$i_L(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

→ form of solution remains same for the complete circuit.

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \quad 5$$

$A_1 ?$

$A_2 ?$


$$i_L(t=0) =$$

$$\frac{di_L}{dt}(t=0) =$$

Initial conditions


$$t < 0$$
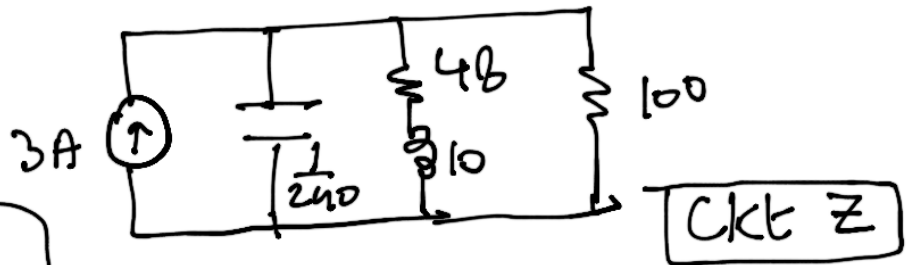
$$Ckt Z \text{ at } t \rightarrow \infty = Ckt A \text{ at } t = 0$$




$$t = -\infty$$
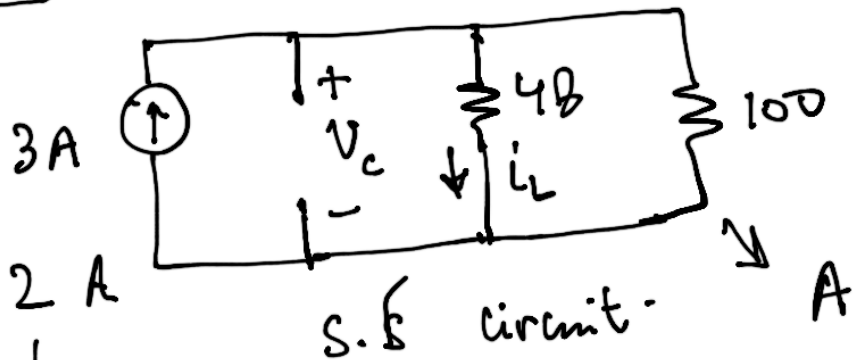
$$i_L(t = \infty)_Z = \frac{100}{140} \times 3A = 2A$$



$$V_C(t = \infty)_Z = 4 \times 2 = 97V$$

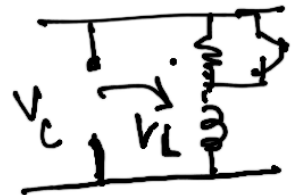

For Ckt A  $\rightarrow$

$$i_L(t = 0)_A = i_L(t = \infty)_Z = 2A$$

$$V_C(t = 0)_A = V_C(t = \infty)_Z = 97V$$

$$i_L = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t) \quad \text{--- (1)}$$

$$t = 0 \quad 2 = e^{-\alpha \cdot 0} (A_1 + 0) \Rightarrow A_1 = 2 \quad \text{--- (2)}$$

$$\frac{di_L}{dt} = e^{-\alpha t} (-A\omega_d \sin \omega_d t + A\omega_d \cos \omega_d t) - \alpha e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t) \quad \text{--- (3)}$$

$$V_C(t=0) = V_L(t=0) \quad \because \text{40 } \Omega \text{ was shared}$$

$$\therefore \textcircled{3} \quad L \frac{di}{dt} = L \left[ e^{-\alpha t} \left( \begin{matrix} \cdot \\ + \end{matrix} \right) - \alpha e^{-\alpha t} \left( \begin{matrix} \cdot \\ + \end{matrix} \right) \right]$$

$$L \frac{di}{dt}(t=0) = L (A_2 \omega_d - \alpha A_1) = 97 \quad \text{---} \textcircled{3'}$$

Solve  $\textcircled{3'}$  to find  $A_2$

$$i_L = e^{-1.2t} \left( 2.027 \cos(4.7t) + 2.56 \sin(4.75t) \right)$$

