
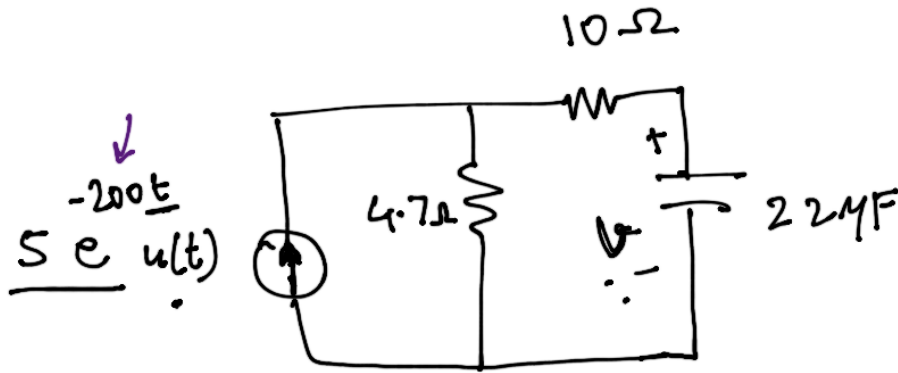


20 Jan

Ex

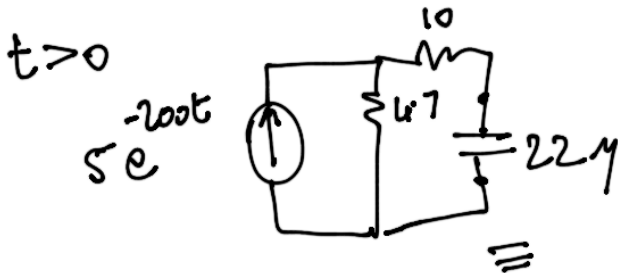

Find $V(t)$



$$V = V_f + V_n - t/\tau$$

$$V = V_f + A e^{...}$$

' τ '

$$C = 22 \mu F$$

$$R \text{ across } C = ? \quad R_{th} = 14.7$$




$$\tau = RC$$

$$= 14.7 \mu s \cdot 22 \mu F = \underline{\hspace{2cm}}$$

* V_s or I_s is constant \rightarrow Forced is also constant (s.s response)

V_s or I_s is changing, the Forced is also a function of time.

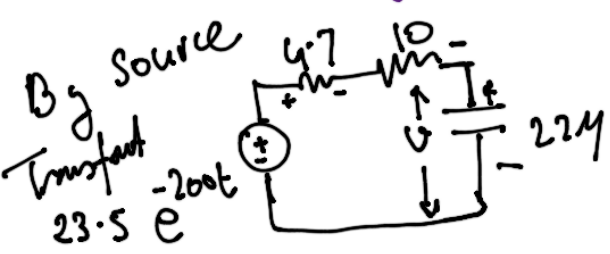Method 1 write KVL or KCL & solve differential equation.
(by first principle)



$$23.5 e^{-200t} = \left(22 \mu \frac{dV}{dt} \right) (4.7 + 10) - V = 0$$

$i = C \frac{dV}{dt} \Rightarrow$ Solve this Diff eq.

Solve the 1st ODE

$$V = - \int \frac{1}{-2000t} dt + A e^{-t/\tau}$$


$$= K \frac{e^{-2000t}}{-2000} + A e^{-t/\tau}$$

$$V = \frac{K e^{-2000t}}{\text{Forced}} + \frac{A e^{-3092t}}{\text{Natural}}$$


$$V = - e^{-2000t}$$

C R

L R

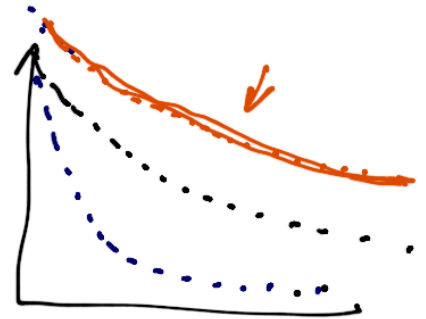

RLC

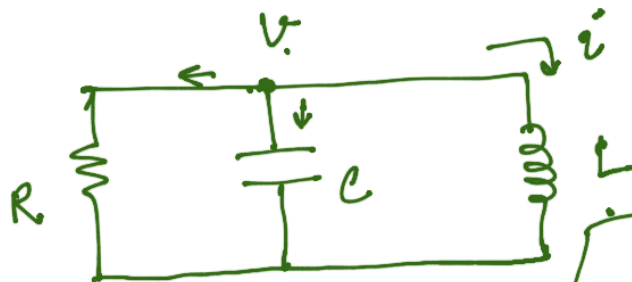

$$V_L = L \frac{di}{dt}$$
$$\Rightarrow i = \frac{1}{L} \int V_L dt$$

KCL

$$-\frac{V}{R} - C \frac{dV}{dt}$$

$$- \frac{1}{L} \int V dt = 0$$

Differentiate it wrt 't'

$$\rightarrow \frac{1}{R} \frac{dV}{dt} + C \frac{d^2 V}{dt^2} + \frac{1}{L} V = 0 \quad \text{--- [A]}$$

2nd ODE

Borrowing solution of 2nd ODE from Mathematics

≡ Solution of ODE is abt $V = \frac{A e^{st}}{s' \rightarrow \text{constant}}$

Substituting $A e^{st}$ into [A]

$$\frac{1}{R} A s e^{st} + C A s^2 e^{st} + \frac{1}{L} A e^{st} = 0$$
$$\left(C s^2 + \frac{s}{R} + \frac{1}{L} \right) A e^{st} = 0$$

Characteristic Equation

$$\text{Solve } C s^2 + \frac{1}{R} s + \frac{1}{L} = 0$$

$$CS^2 + \frac{S}{R} + \frac{1}{L} = 0$$

$$S = \frac{-\frac{1}{R} \pm \sqrt{\frac{1}{R^2} - 4 \cdot \frac{C}{L}}}{2C}$$

$$S = \frac{-\frac{1}{2RC} \pm \frac{1}{2} \sqrt{\frac{1}{R^2 C^2} - \frac{4}{LC}}}{1}$$

Solutions

$$\begin{aligned} S_1 &= -\frac{1}{2RC} + \sqrt{\frac{1}{(2RC)^2} - \frac{1}{LC}} \\ S_2 &= -\frac{1}{2RC} - \sqrt{\frac{1}{(2RC)^2} - \frac{1}{LC}} \end{aligned} \left. \vphantom{\begin{aligned} S_1 \\ S_2 \end{aligned}} \right\} \begin{array}{l} \leftarrow \\ \rightarrow \text{decay} \end{array}$$

The solution Ae^{st}

$$V = A e^{S_1 t} + B e^{S_2 t} \quad \left. \vphantom{V = A e^{S_1 t} + B e^{S_2 t}} \right\} \text{Solution to R-L-C circuit.}$$

Analyze S_1 & S_2

Let $\frac{1}{2RC} = \alpha$ Damping factor.

$\frac{1}{LC} = \omega_0^2$ Resonant frequency.

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

α, ω_0

$$\alpha > \omega_0$$

$$\alpha = \omega_0$$

$$\alpha < \omega_0$$

s_1

$$-\alpha$$

$$-j\omega$$

s_2

$$-\alpha$$

$$-j\omega$$

Overdamped

Critically damped

Under damped

..