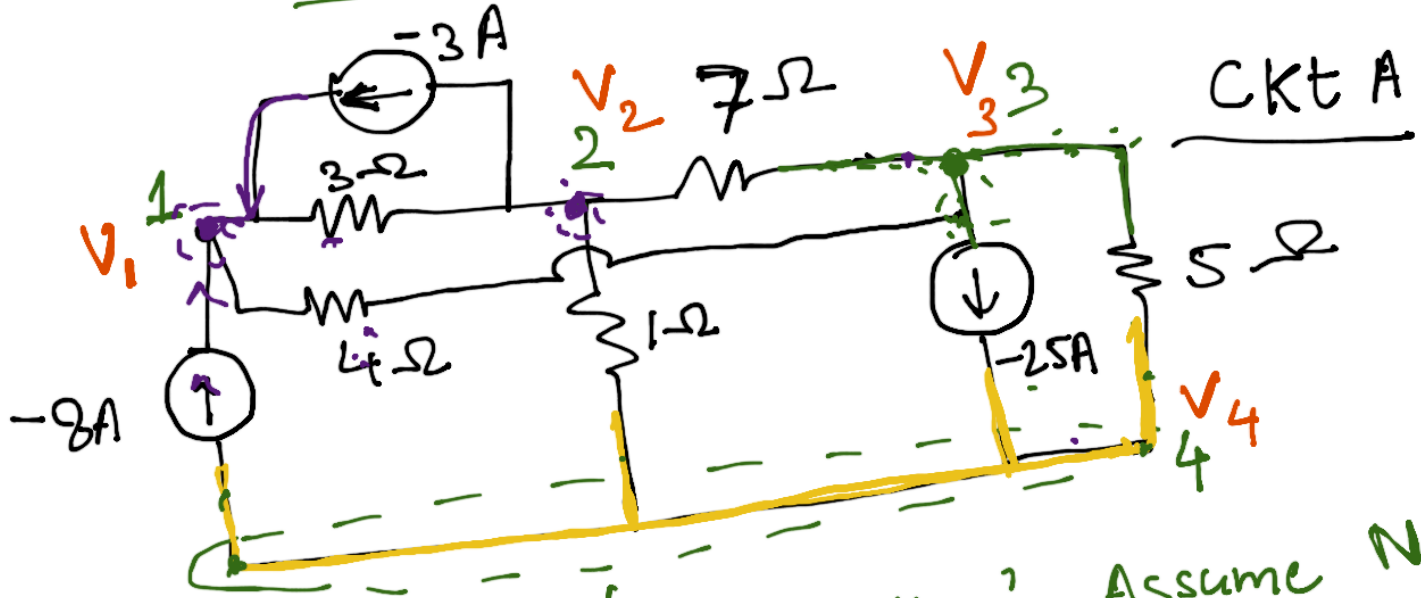


Steps: KCL

KCL



1. Identify Nodes. Node voltage. Assume Node voltage.

2. Determine current flow

3. Write equation at node $\sum i = 0$


$$\textcircled{N1} \text{ KCL} \quad -8A - 3A + \frac{V_2 - V_1}{3} + \frac{V_3 - V_1}{4} = 0 \quad \textcircled{1}$$

$$-8A - 3 = \frac{V_1 - V_2}{3} - \frac{V_1 - V_3}{4} = 0 \quad \textcircled{1}$$

$$\boxed{N2^2, N3^3, N4^4}$$

$$\boxed{V_1 \quad V_2 \quad V_3 \quad V_4}$$

KVL

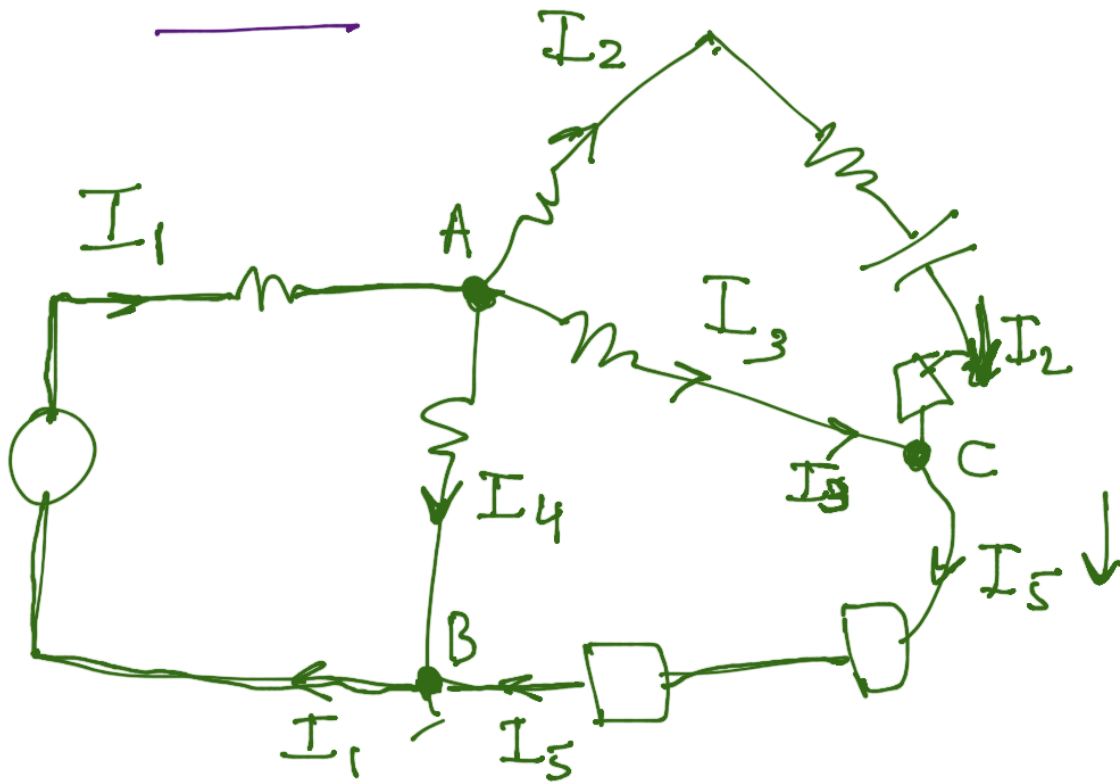

1. Branch currents [KCL]

2. Loop currents $+I_1 - I_2 - I_3 - I_4 = 0$


'A' $\left\{ I_4 = + \left(I_1 - I_2 - I_3 \right) \right.$ $I_1 = I_1 - I_2 - I_3$

Node 'C'

$$\frac{I_2 + I_3 = I_5}{+I_2 + I_3 + (-I_5) = 0}$$

'C'

B $+I_4 + I_5 - I_1 = 0$

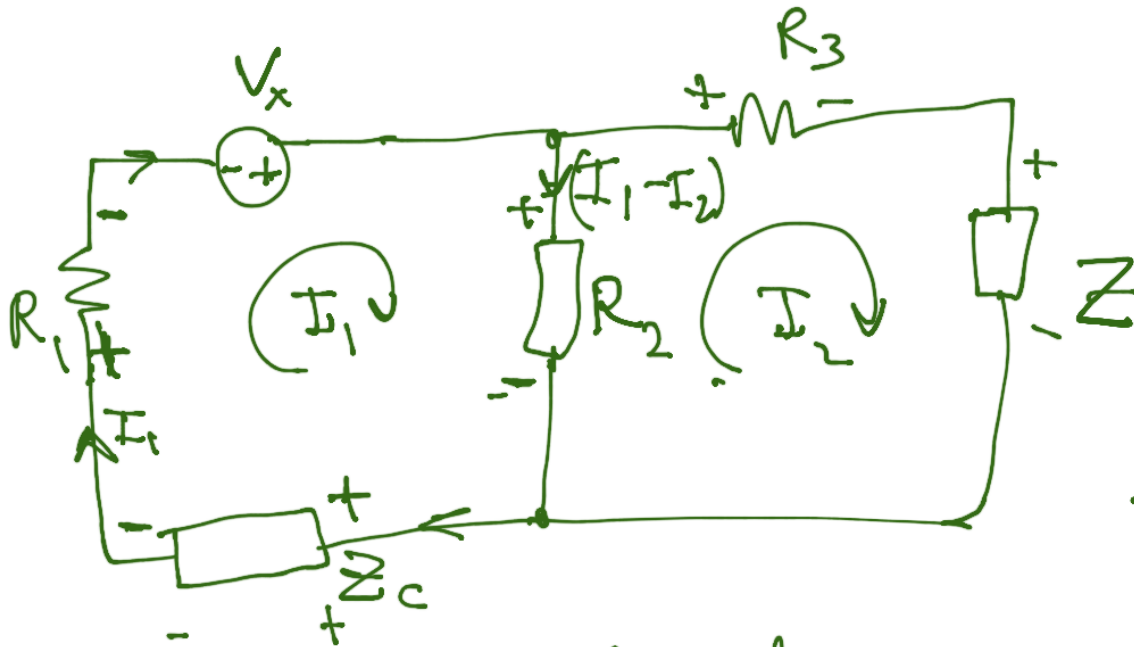

Assign loop current -

& ① KVL


$$- \underbrace{I_1 R_1} + \underbrace{V_x} - (I_1 - I_2) R_2 - \underline{Z_c I_1} = 0$$

$$② \quad + (I_1 - I_2) R_2 - I_2 R_3 - I_2 Z = 0$$

A	B	C	D
8	10	10	10
10	10	10	10
→ 10	10	8	5+
10			

KCL

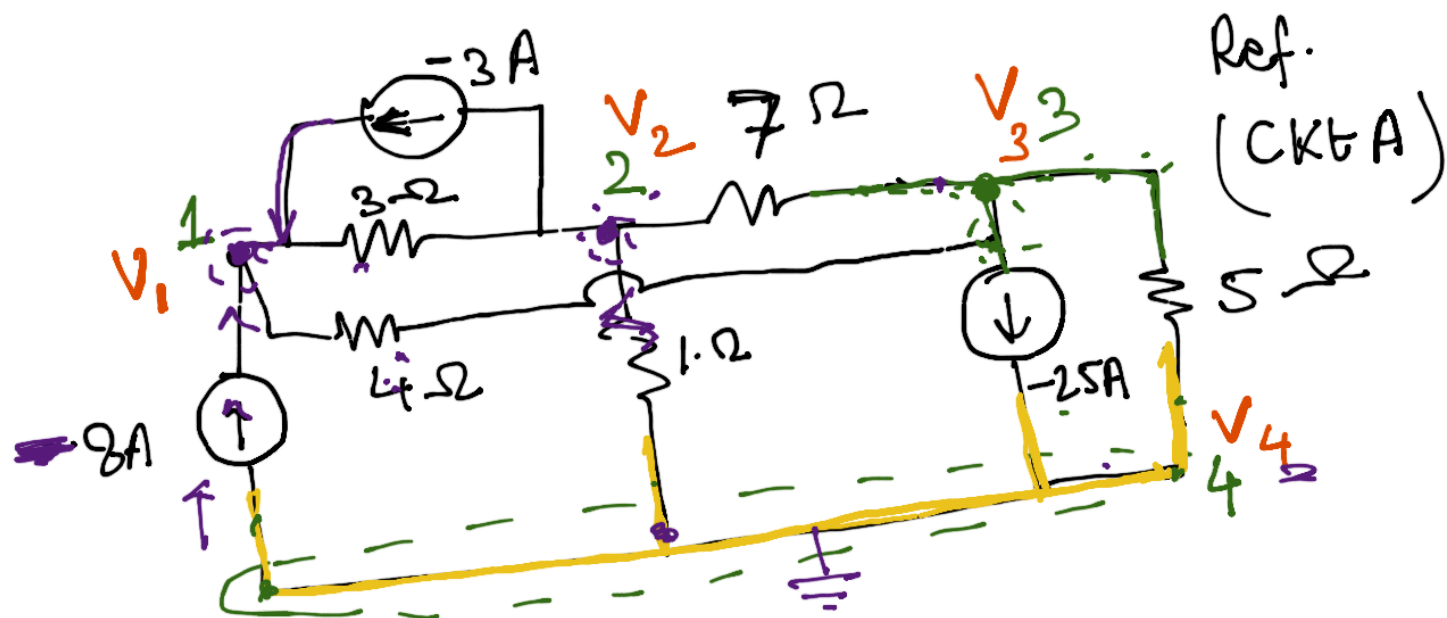1. Identify the node
2. Assign voltages to node (unknown)
3. Balance currents at each node.



N2 $\frac{V_2 - V_1}{3} + \frac{V_2 - V_3}{7} + \frac{V_2 - V_4}{1} = 3$ (2)

N3 $\frac{V_3 - V_2}{7} + \frac{V_3 - V_4}{5} + \frac{V_3 - V_1}{4} + (-25) = 0$ (3)

N4 $\frac{V_4 - V_3}{5} + \frac{V_4 - V_2}{1} + (-4) = -25$ ✓

4 Node & 4 Equations



4 unknown.

Assign a reference node


$V_1, V_2, V_3, V_4, \text{ gnd} = 0$

Reference Node : Any node = GND (zero volt)

Unknown V_1, V_2, V_3
 ξ^n ①, ②, ③ } Algebra

Mesh : Multiple connection of various elements/components in a circuit making different loops.

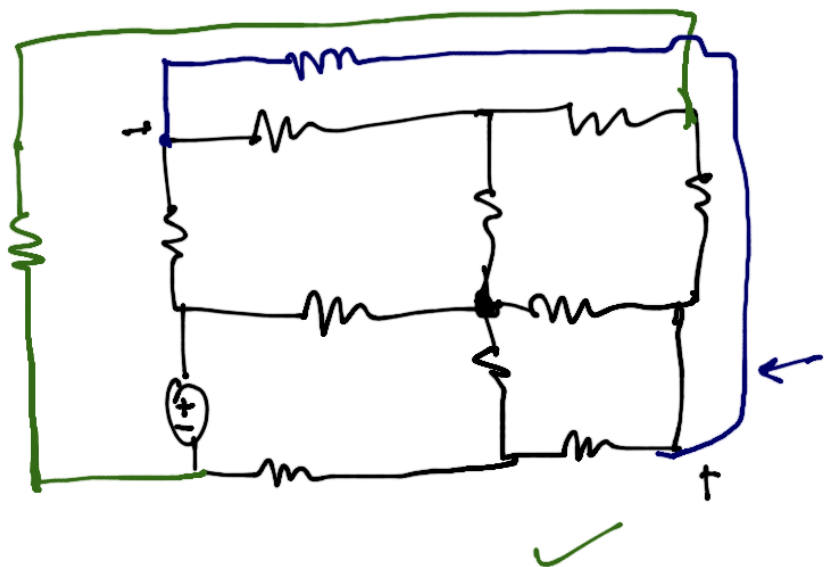Planar circuit : 2 dimensional = planar.
^{in 2D}
Simplify ckt. sk. No branches overlapping i.e..
no branch passes over or under any other branch \rightarrow planar circuit.



Not a planar

