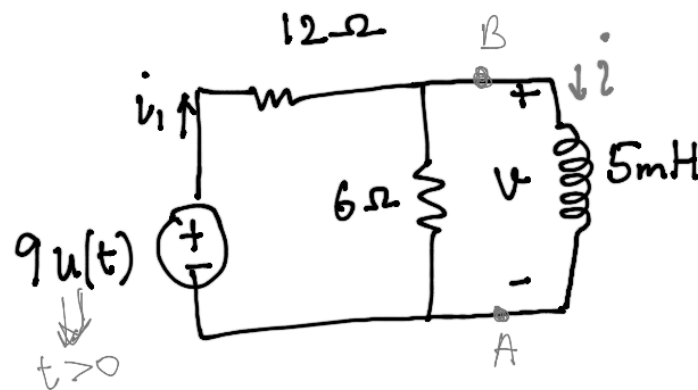


RC & RL circuit examples

Example 1




$$i = ?$$

$$i_1 = ?$$

$$v = ?$$

Solution Inductor can be seen as load and Equivalent Thevenin values

Calculated

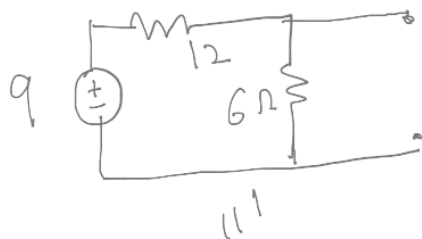

From circuit R_{th} is obvious $R_{th} = 6 \parallel 12$
 $= \frac{72}{18} = 4 \Omega$

$$V_{th} = \frac{6}{18} \times 9 = 3V$$

$$v = A e^{-Rt/L}$$

where $\tau = \frac{L}{R} = \frac{5m}{4} = 1.25ms$

$t=0$ $v=3V$ (all drop is across inductor at $t=0$)

$$\therefore v = 3 e^{-\frac{t}{1.25 \times 10^{-3}}} \Rightarrow i(t) - i(0) = \frac{1}{5m} \int_0^t v dt =$$



$$i(t) - i(0) = \frac{1}{5m}$$

$$\begin{aligned} & \parallel \\ & i(t) \\ & [as\ i(0)=0] \end{aligned}$$

\Rightarrow

$$\int_0^t 3 e^{-\frac{t}{1.25m}} dt = \frac{1}{5m} * 3 \left(\overset{0.25}{\cancel{1.25m}} \right) \left(e^{-\frac{t}{1.25m}} - 1 \right)$$


$$i(t) = 0.75 * \left(1 - e^{-t/1.25m} \right)$$

$$i_1 = \frac{9V - v(t)}{12\Omega} = \frac{9 - 0.75 \left(1 - e^{-\frac{t}{1.25m}} \right)}{12}$$

$$= \frac{3}{4} - \frac{1}{4 \times 4} e^{-t/1.25ms} = \boxed{\frac{3}{4} - \frac{1}{16} e^{-\frac{t}{1.25ms}} = i_1(t)}$$

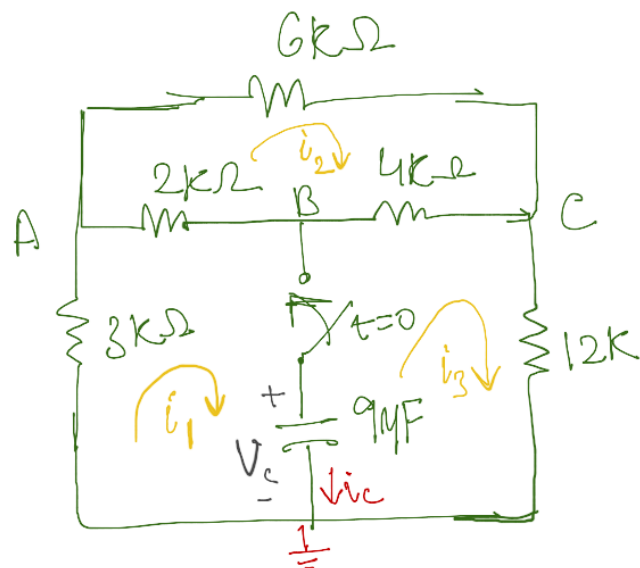Example 2

$$R_{eq} = R_{th} = \frac{V_B}{-i_c} = \frac{V_B}{(i_3 - i_1)}$$



$$V_C(t=0) = 17V$$

Find V_A , V_B , V_C , all currents.

Solution: we write KCL or KVL for the circuit for $t > 0$

$$\text{KVL } (i_1) \quad -3K i_1 - 2K (i_1 - i_2) - V_C = 0 \quad \text{---(1)}$$

$$\Rightarrow -5K i_1 + 2K i_2 - V_C = 0$$

$$(i_2) \quad -6K i_2 - 4K (i_2 - i_3) - 2K (i_2 - i_1) = 0$$

$$\Rightarrow 2K i_1 - 12K i_2 + 4K i_3 = 0 \Rightarrow i_1 - 6i_2 + 2i_3 = 0 \quad \text{---(2)}$$

$$(i_3) \quad V_C - 4K (i_3 - i_2) - 12K i_3 = 0 \quad \text{---(3)}$$

$$\Rightarrow 4K i_2 - 16K i_3 + V_C = 0$$

check sign

Solve (1), (2) & (3) for i_1 , i_2 , i_3

$$i_1 = -\frac{21}{118K} V_C \quad \text{(4)}$$

$$i_2 = \frac{13}{236K} V_C \quad \text{(5)}$$

$$i_3 = \frac{9}{118K} V_C \quad \text{(6)}$$

$$E.g. \text{ resistance across cap} = \frac{-V_C}{(i_1 - i_3)} = \frac{-V_C}{(-21 - 9)V_C / 118K} = +\frac{118K}{30} = R_{th}$$

$$\tau = R_{eq} * C = \frac{118K}{21} * 9\mu F = \frac{118 * 10^3}{21} m \text{ seconds}$$

$$\tau = \frac{354}{7} m \text{ seconds}$$

General solution

$$\therefore V_c(t) = A \cdot e^{-t/\tau}$$

$$t=0 \quad V_c = 17$$

$$\therefore V_c = 17 e^{-t/\tau}$$

$$\Rightarrow i_c = C \frac{dV_c}{dt} = 9\mu * \frac{17K}{(354/7)} e^{-t/\tau} = i_c$$

$$= 3.025 \times 10^{-3} e^{-t/\tau}$$

$$\text{Using (4): } i_1 = -\frac{21}{118K} * 17 e^{-t/\tau}$$

$$\text{Using (5): } i_2 = \frac{13}{236K} * 17 e^{-t/\tau}$$

Value of all currents.

$$\text{Using (6): } i_3 = \frac{9}{118K} * 17 e^{-t/\tau}$$

$$V_A = V_B = V_c + 2K * (i_1 - i_2) = 17 e^{-t/\tau} + 2K * (i_1 - i_2) =$$

$$V_C = V_B + 4K(i_2 - i_3) = 17 e^{-t/\tau} + 4K * (i_1 - i_2) =$$

Extra credits to one who finds calculation mistake & updates value of V_A & V_C .

Example 2+

In the previous problems find the steady state values.

Solution(1): For steady state values $t \rightarrow \infty$ in the obtained solutions.

Solution(2): Take $L \rightarrow$ short (zero resistance wire = zero voltage drop).
and $C \rightarrow$ open (zero current flow).

Repeat the calculations.