
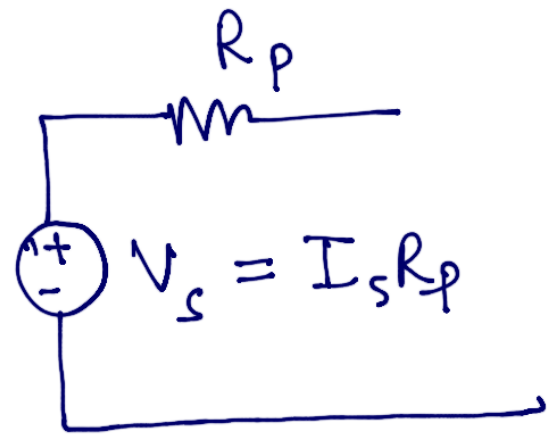


Current Source

\equiv

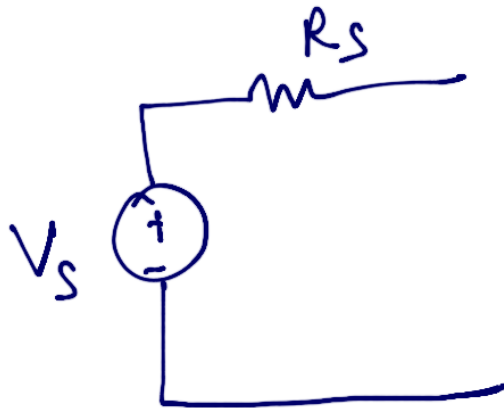


Voltage Source




Voltage Source

\equiv

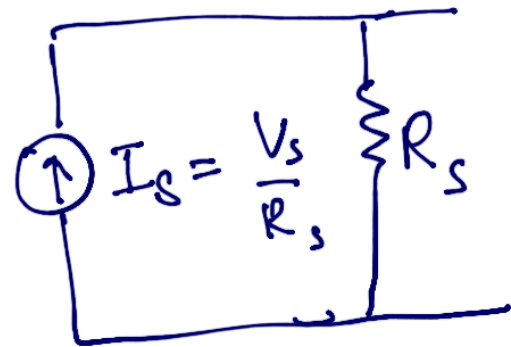

Source Transformation


Summary

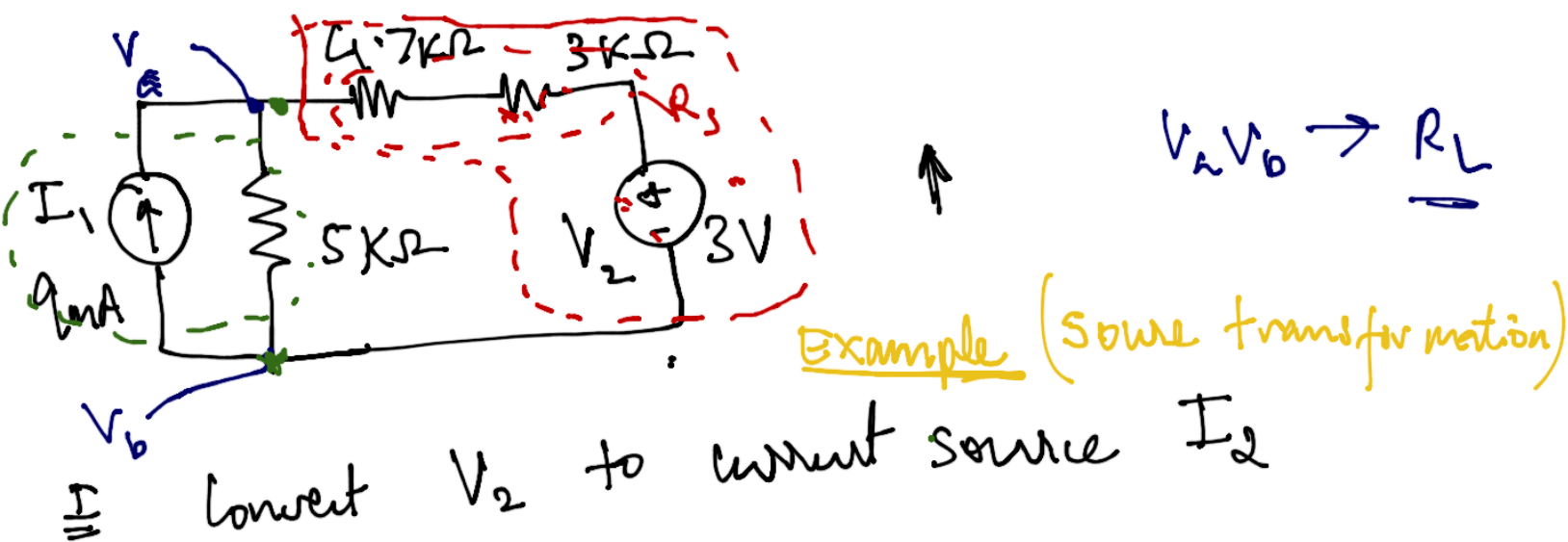

Convert V_2 to current source I_2

$$I_2 = \frac{V_2}{4.7k + 3k} = \frac{3}{7.7k} = 0.39 \text{ mA}$$

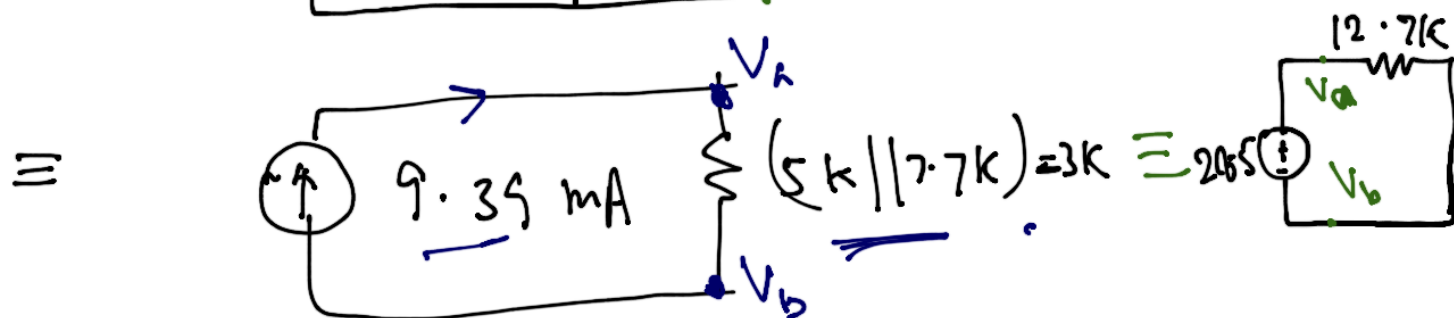
$$R_{P2} = 4.7k + 3k\Omega = 7.7k\Omega$$



Convert I_1 to V_1 voltage source



$$V_1 = I_1 \times R_p = 9\text{mA} \times 5k\Omega = 45V$$

$$R_{S1} = 5k\Omega$$

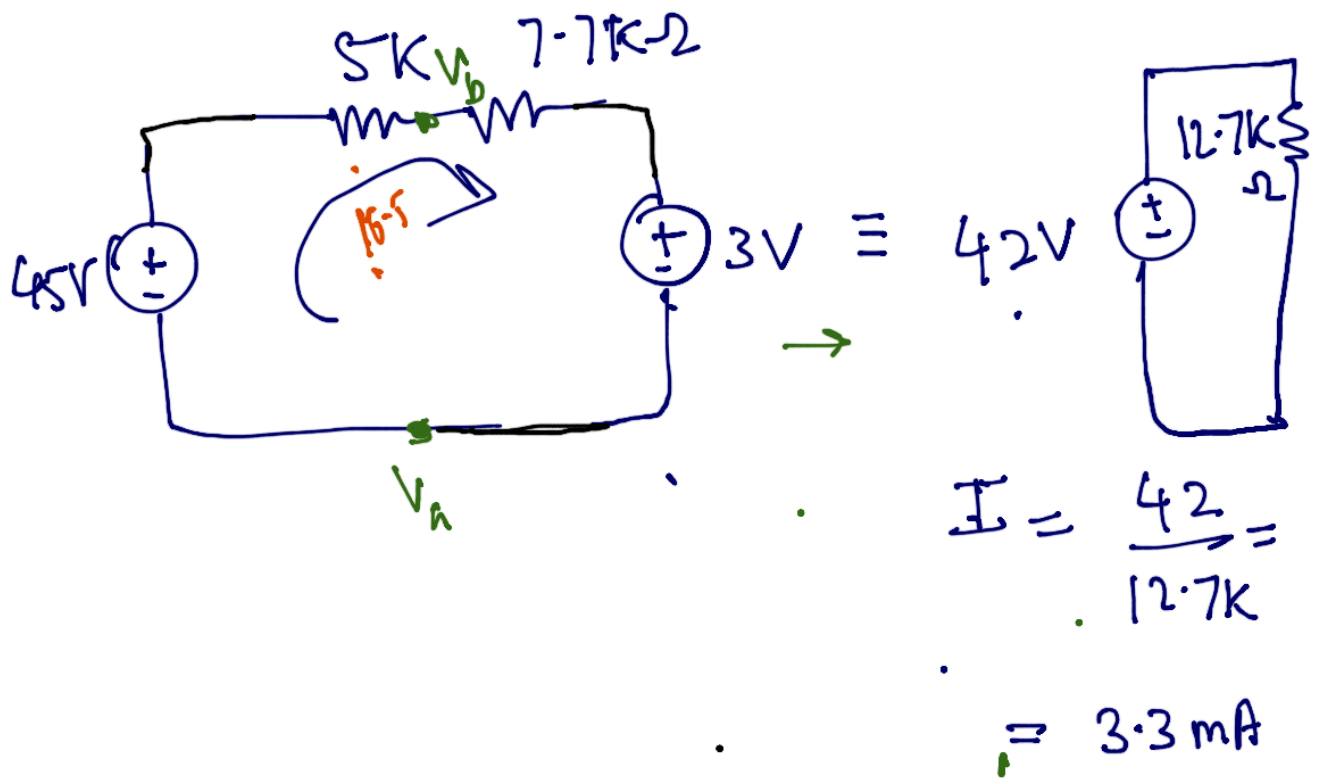


Norton & Thevenin Circuits

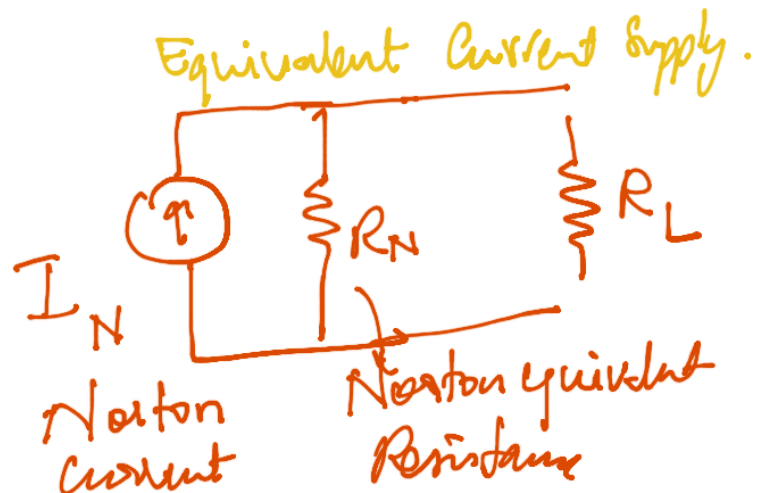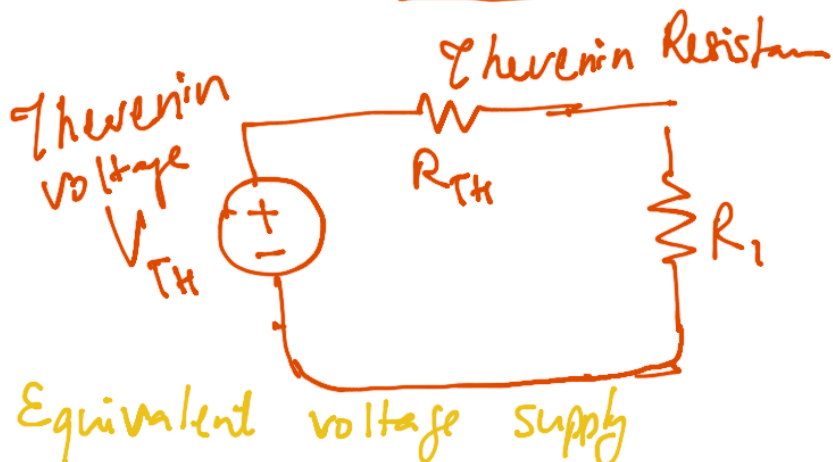Supply System can be simplified across the load terminals.





Example

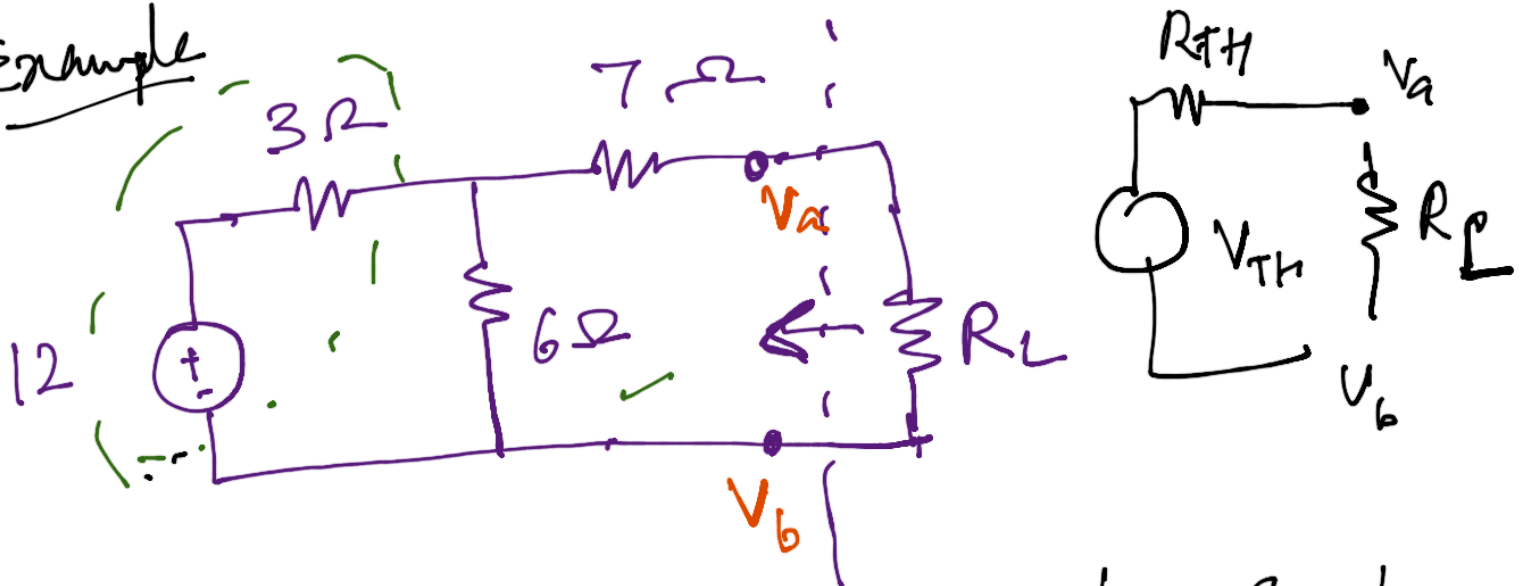


→ Between V_a & V_b what is the supply
 (V_{TH}, R_{TH}) or (I_N, R_N) ?

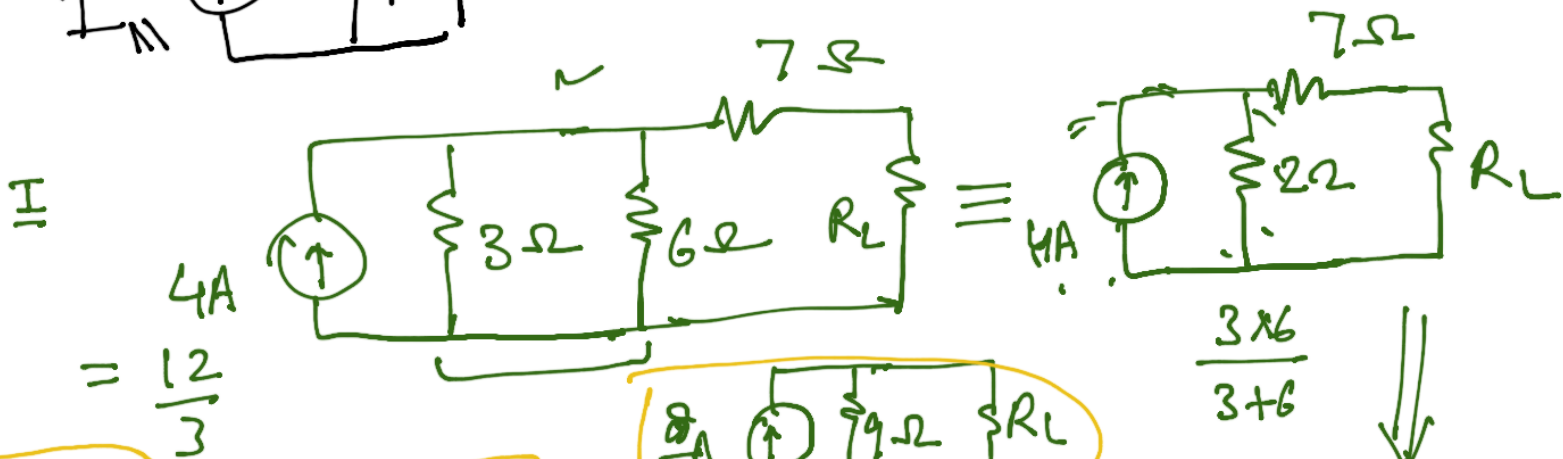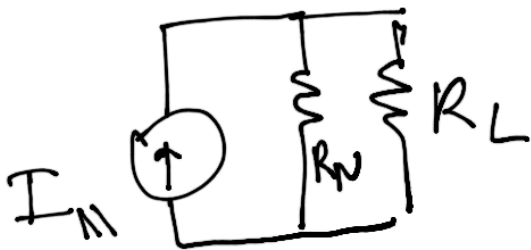
*Thevenin & Norton are
 equivalent & interchangeable.*



$V = 8V$
 8×2

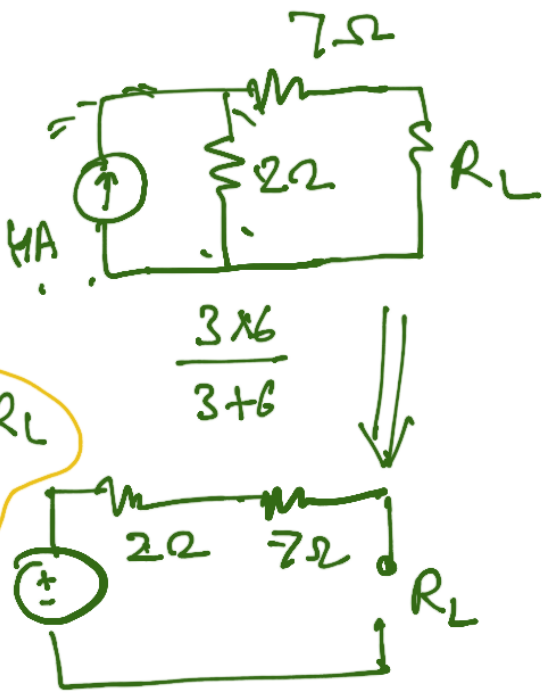

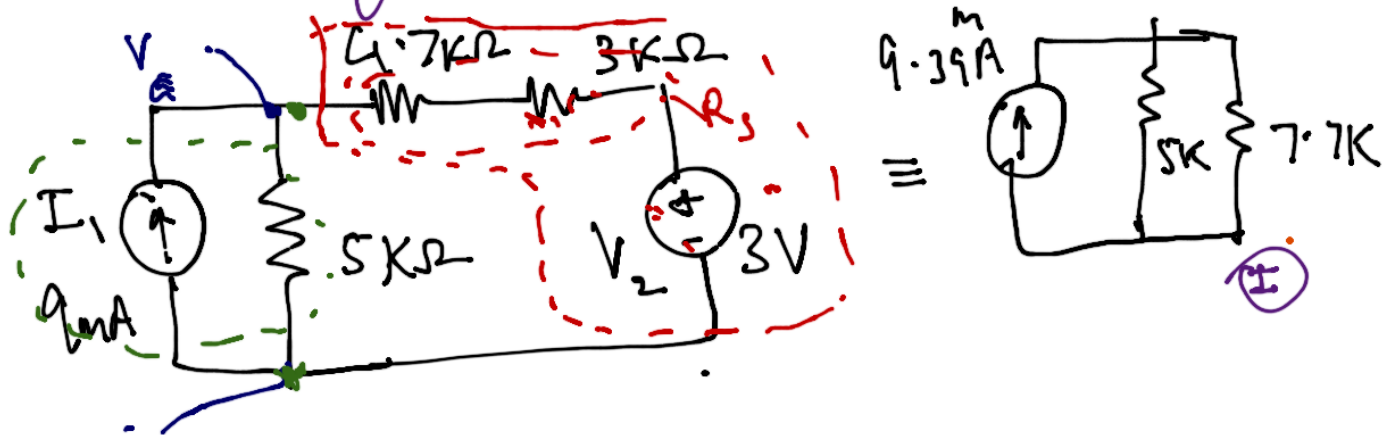Revisiting Circuits to evaluate drop across 5K




Voltage across 5K in (I) Epi ckt. $= \frac{7.7}{5+7.7} * 9.39 * 5K$

$= \underline{28.46 V}$

Voltage across 5K in (II) Epi ckt $= \underbrace{V_a - V_b}_{(V_a - V_b)} = 3 + 7.7K * \frac{42}{5K+7.7K} = 3 + \frac{7.7K * 42}{12.7}$

$= 3 + 25.46 = \underline{28.46V}$

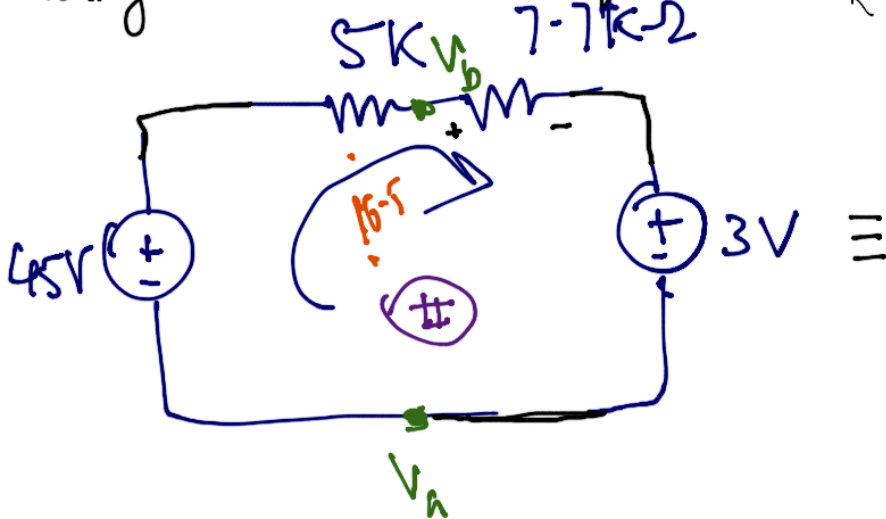

The drop across V_a & V_b points (original terminals of 5K) is same in both the simplification process.

HW: Please use KCL, KVL and verify the $(V_a - V_b)$ also.