

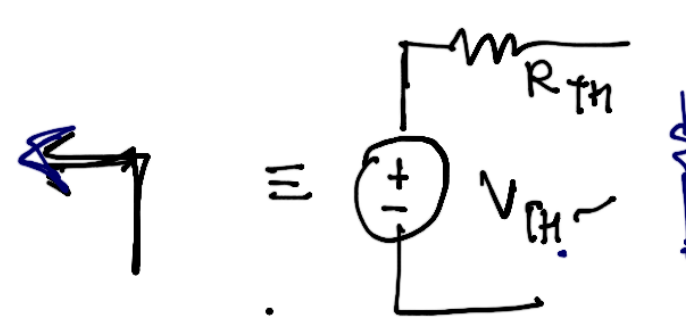


Ex 5.7

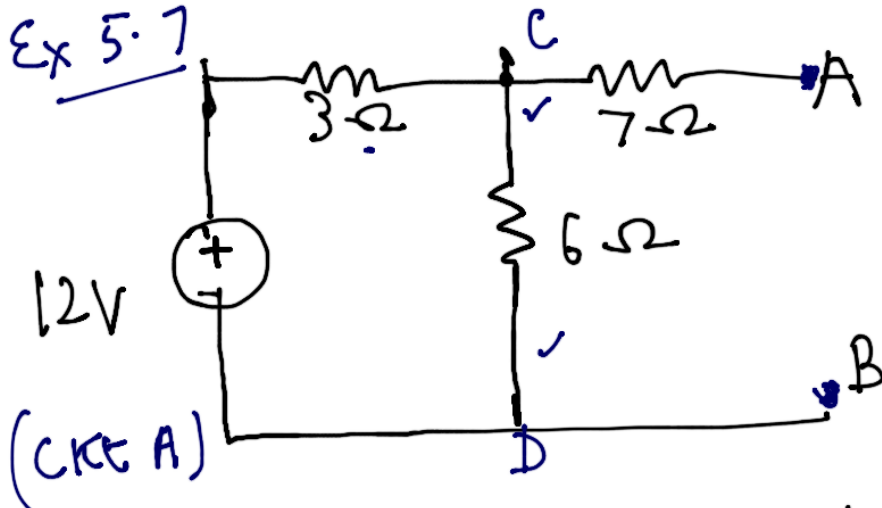

Find Thevenin equivalent between A & B

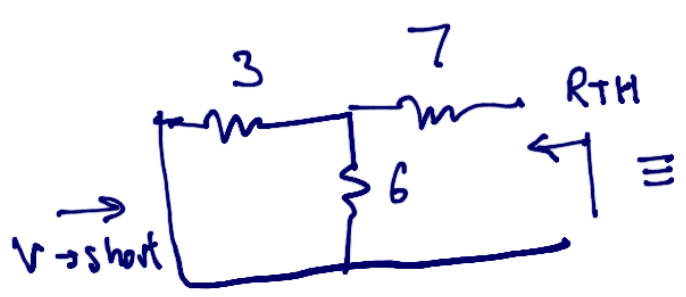Step 1 R_{th} . Make current/voltage source = 0
 $V_{source} \rightarrow$ Short Circuit
 $I_{source} \rightarrow$ Open Circuit




$2 \times \left\{ \begin{matrix} 3\Omega \\ 6\Omega \end{matrix} \right\} + 7\Omega \rightarrow R_{TH} \Rightarrow R_{TH} = 9\Omega$

Step 2 V_{TH} . Find V_{AB}

In Ckt A $V_{CD} = V_{AB}$; $V_{CD} = \frac{6\Omega}{6\Omega + 3\Omega} * 12$

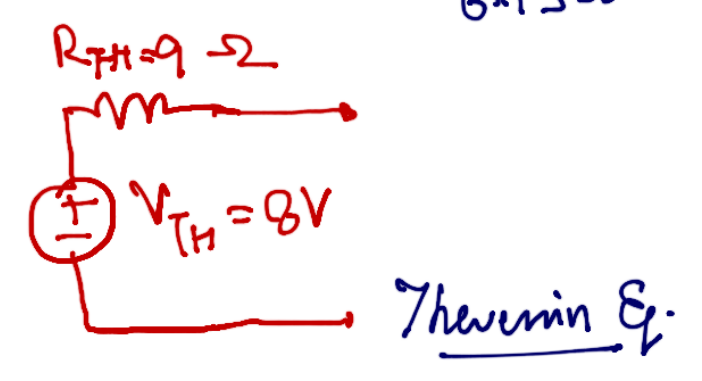
$V_{AB} = V_{TH} = V_{CD} = \frac{2}{3} * 12 = 8V$



Thevenin Eq.


Steps : Thevenin Eq.

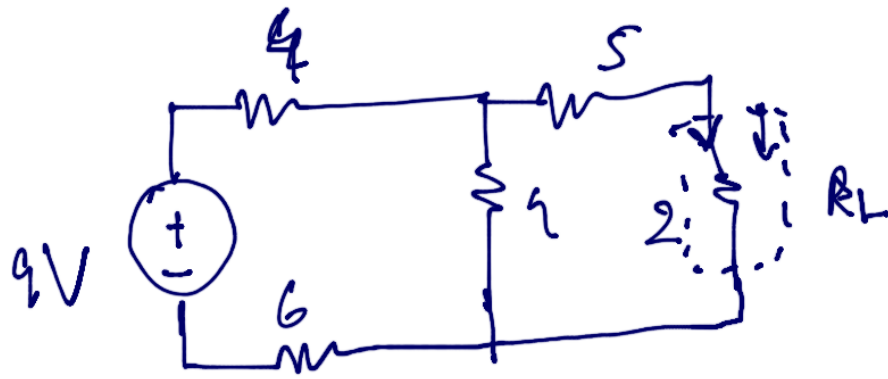- 1(a) Know the terminals ^(AB) across which Equivalent has to be calculated.
- 1(b) Remove the load put
- 2 ~~R_{TH}~~ All independent sources $\rightarrow 0$
i.e. Voltage sources \rightarrow Short Ckt. (S.C)
Current sources \rightarrow Open Ck (O.C)
Leave dependent sources as they are.
- 2(b) Find the Equivalent Resistance between A & B.
3. Find voltage V_{AB} across the two terminals.




S.6 Practice

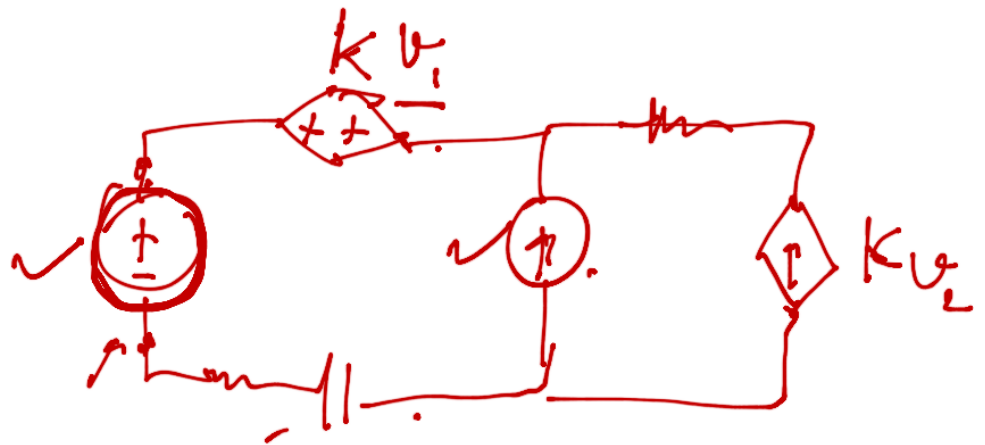* In Superposition Theorem, we consider only independent voltage/current source.




Norton Equivalent

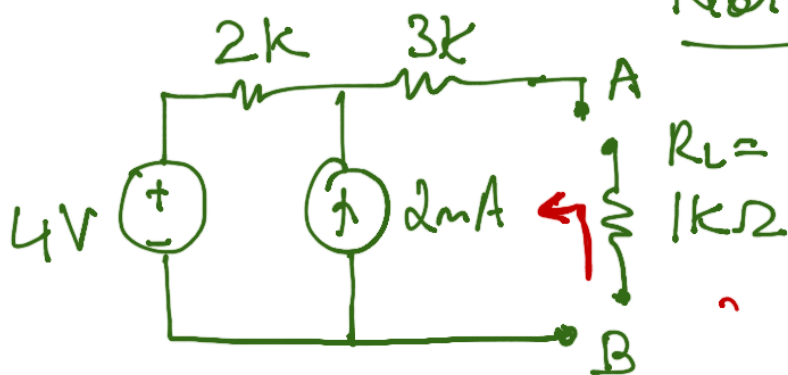

Step 1 Find R_N : $V \rightarrow$ S.C


$I_{source} \rightarrow$ O.P

& Solve.

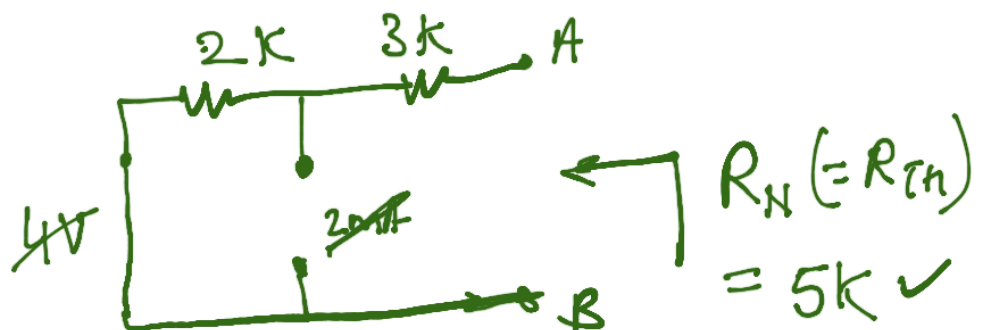


Step 2 I_N

S.C Terminals AB

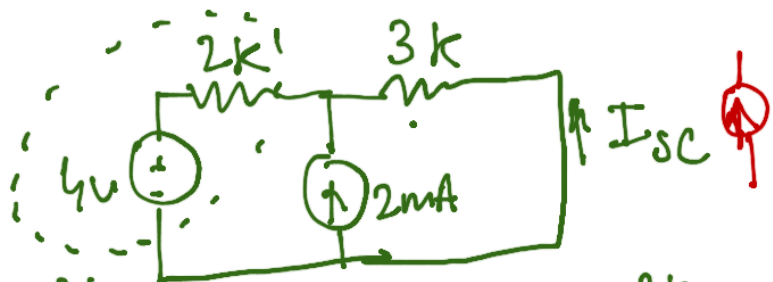

KVL, KCL, Superposition

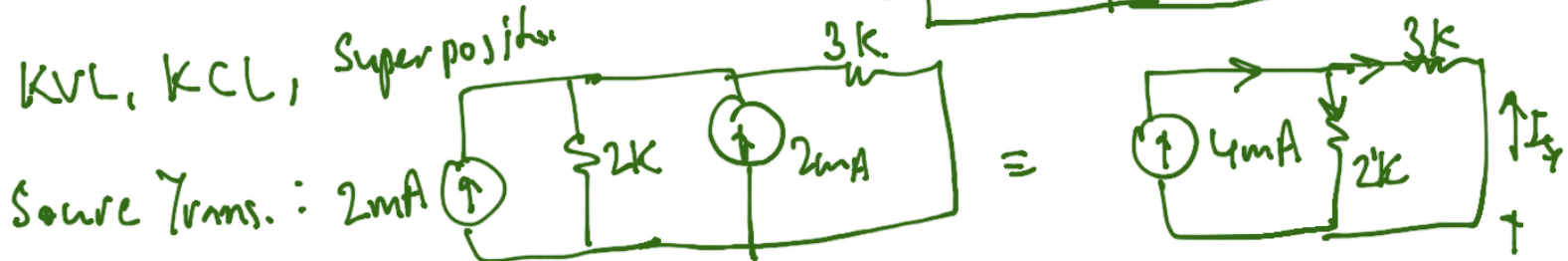

$$\Rightarrow I_{sc} = -\frac{2}{5} \times 4\text{mA} = -\frac{8}{5}\text{mA} = -1.6\text{mA}$$

Steps for Norton Equivalent


1(a) Find the terminals across which R_N , I_N have to be found.

(b) Remove R_L



2. R_N
(a) Independent $\left\{ \begin{array}{l} V_{\text{open}} \rightarrow \text{S.C} \\ I_{\text{open}} \rightarrow \text{O.C} \end{array} \right.$

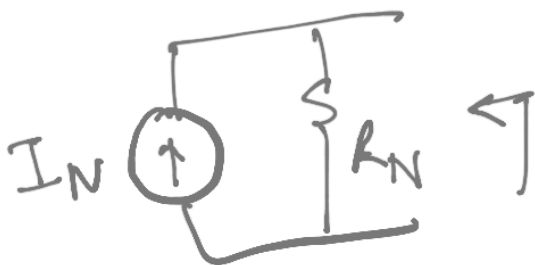(b) Find Equivalent Resistance across the terminals

3 I_N
Short circuit the terminals & find the short circuit current I_{sc} across the terminals. This is I_N



Maximum Power Transfer Theorem

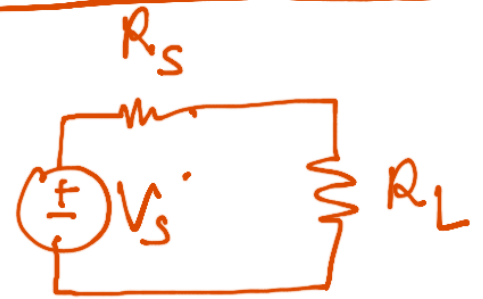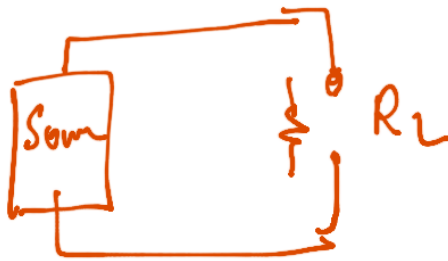


Power transferred to the load = P_L

Plot the power vs R_L

$$\rightarrow \frac{\partial P_L}{\partial R_L} = 0$$

R_L in terms known value.

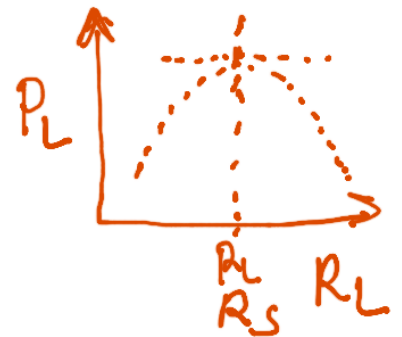


$$R_s = R_L :$$

$$P_{L_{max}} = ?$$

Chapter 7


A	B	C	D
10	10	10	10

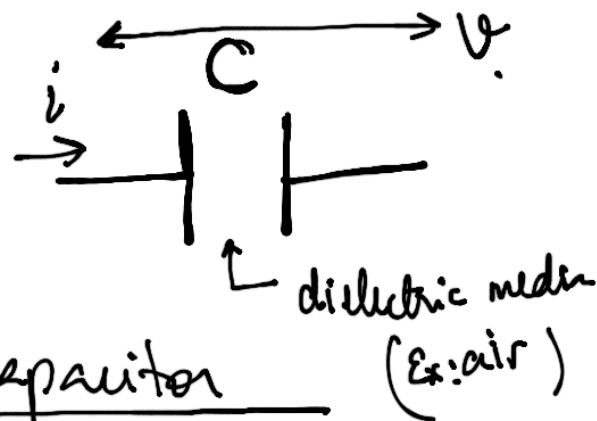

- Capacitor
- Stores Charge
 - Two parallel metal plates
 - Both plates have opp. Charge.


- V is applied across the cap

What is $i_c = C \frac{dV}{dt}$

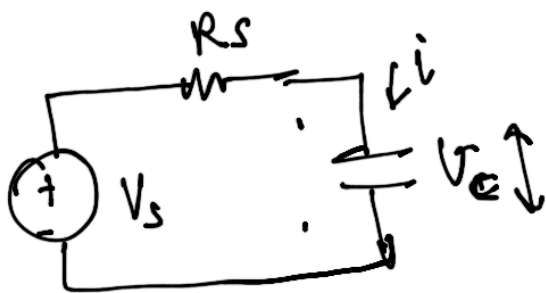

$$i = C \frac{dV}{dt}$$

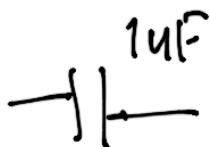- Charge stored per unit voltage $C = \frac{Q}{V}$
Unit: Farad (F)



$$\text{power} = V i = V_c C \frac{dV_c}{dt}$$

Current-Voltage Relationship

$$i = C \frac{dV}{dt}$$

$$\int_{t_0}^t \frac{dV}{dt} dt = \frac{1}{C} \int_{t_0}^t i dt.$$

$$V(t) - V(t_0) = \frac{1}{C} \int_{t_0}^t i dt$$

$t_0 \rightarrow$ starting / initial time

\uparrow

$Q-V$ Relationship

$$Q = C V$$

↓
Capacitance

Ex 7.1, 7.2.
Practice \rightarrow 7.2

Energy & Power of a Cap

$$\text{Power} = C v_c \frac{dv_c}{dt}$$

$$\begin{aligned} \text{Energy} &= \int_{t_0}^t P \cdot dt \\ &= C \int_{t_0}^t v_c \frac{dv_c}{dt} \cdot dt \end{aligned}$$


$$= C \int_{t_0}^t v_c \, dv_c = C \left[\frac{v_c^2}{2} \right]_{v_c(t_0)}^{v(t)}$$

$$\text{Energy} = \frac{C}{2} \left[v_c^2(t) - v_c^2(t_0) \right]$$

If initial v_c at t_0 ($v_c = 0$)

$$\text{Energy} = \frac{1}{2} C v_c^2(t)$$

Inductor

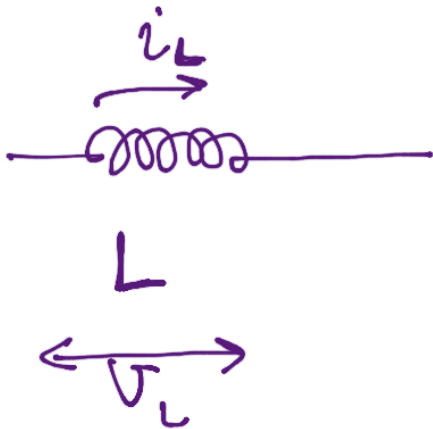

$$V_L = L \frac{di_L}{dt}$$

$L \rightarrow$ inductor

'Inductance'

Units: Henry (H)

Current ~ Voltage Relation.

$$\int_{t_0}^t di_L = \frac{1}{L} \int_{t_0}^t V_L dt$$

$$i_L(t) - i_L(t_0) = \frac{1}{L} \int_{t_0}^t V_L dt$$

Energy Storage

$$\text{Power} = p = v \cdot i$$

$$p_L = v_L i_L$$

$$= L \frac{di_L}{dt} \cdot i_L$$

$$\text{Energy} = \int_{t_0}^t p_L \cdot dt = L \int_{t_0}^t i_L \frac{di_L}{dt} dt$$

$$= L \left[\frac{i_L^2}{2} \right]_{i_L(t_0)}^{i_L(t)}$$

$$\text{Energy} = \frac{L}{2} (i_L^2(t) - i_L^2(t_0))$$

Stored in an inductor

$$W_L = \frac{1}{2} L i^2 \text{ (if initial condition is zero)}$$